

國立中央大學八十六學年度碩士班研究生入學試題卷

所別: 光電科學研究所 不分組 科目:

電子學

共 2 頁 第 1 頁

1. For the collector-coupled flip-flop as shown in Figure 1. Assume transistor Q_1 is the same as Q_2 , $V_{CC} = 10\text{ V}$, $R_C = 1\text{ k}\Omega$ and $R_B = 20\text{ k}\Omega$, the test condition for a flip-flop is "do two stable states exist, in each of which at least one transistor is not active?" to estimate the required minimum β of transistor. (20分)

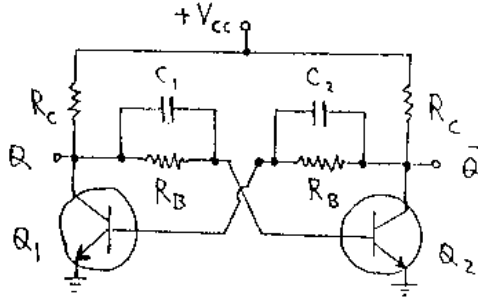


Figure 1.

2. For the FET amplifier as shown in Figure 2. Assume $R_1 = 20\text{ k}\Omega$, $R_2 = 80\text{ k}\Omega$, $R_D = 10\text{ k}\Omega$ and $g_m = 4 \times 10^{-3}\text{ mhos}$, To find the gain without and with feedback. (20分)

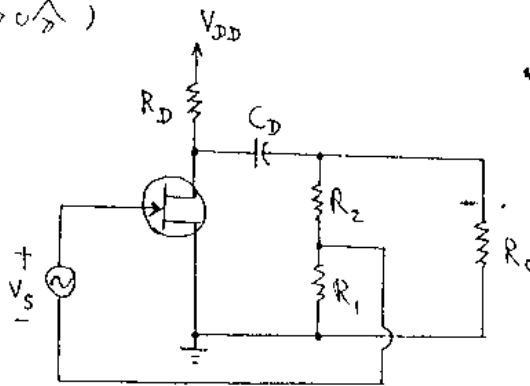


Figure 2.

3. A FET common-source amplifier has $R_{in} = 2\text{ k}\Omega$, $g_m = 4\text{ mA/V}$, $Y_o = 100\text{ k}\Omega$, $R_D = 10\text{ k}\Omega$, $C_{gs} = 2\text{ pF}$, and $C_{gd} = 0.5\text{ pF}$, The amplifier is fed from a voltage source with an internal resistance of $500\text{ k}\Omega$ and is connected to a $10\text{ k}\Omega$ load. Find:
- the overall midband gain A_M (10分)
 - the dominant high frequency pole using the Miller approximation. (10分)
4. (a) Given the circuit of Fig 4 (a) with $\alpha_o = 0.9$ and $I_{E0} = I_{C0} = 1 \times 10^{-5}\text{ A}$ find the critical emitter current that just saturates the transistor. (10分)
- b) From the typical output CE characteristics curves of a

國立中央大學八十六學年度碩士班研究生入學試題卷

所別: 光電科學研究所 不分組 科目: 電子學 共 2 頁 第 2 頁

TIS 100 transistor shown in Fig. 4(b) determine the dc value of β (i.e. h_{FE}) and dynamic value of β (i.e. h_{fe}) at an $I_B = 1.5 \times 10^{-4} A$ and a $V_{CE} = 6 V$. (10分)

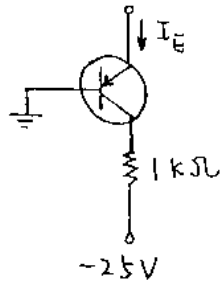


Figure 4(a)

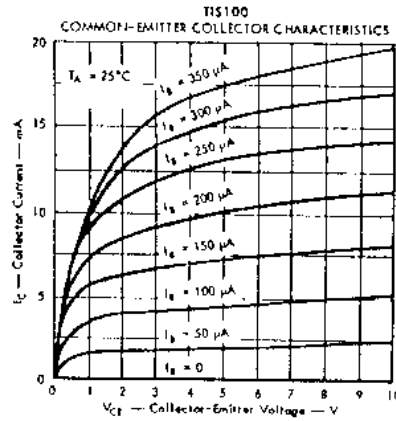


Figure 4(b)

5. An op amp with an open-loop voltage gain of 80 dB and poles at 10^5 , 10^6 , and 2×10^6 Hz is to be compensated to be stable for unity β . Assume that the op amp incorporates an amplifier equivalent to that in Fig. 5, which $C_1 = 150$ pF, $C_2 = 5$ pF, and $g_m = 40$ mA/V, and that f_{p1} is caused by input circuit and f_{p2} by the output circuit of this amplifier. Find the required value of the compensating Miller Capacitance C_f and the new frequency of the output pole. (20分)

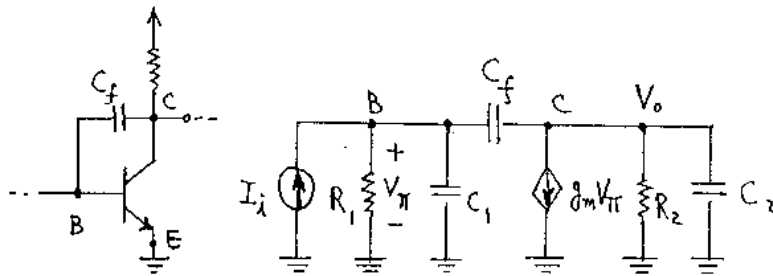


Figure 5