

# 國立中央大學八十四學年度碩士班研究生入學試題卷


所別: 光電科學研究所

組 科目: 電子學



共 2 頁 第 / 頁

共五題, 每題 20 分

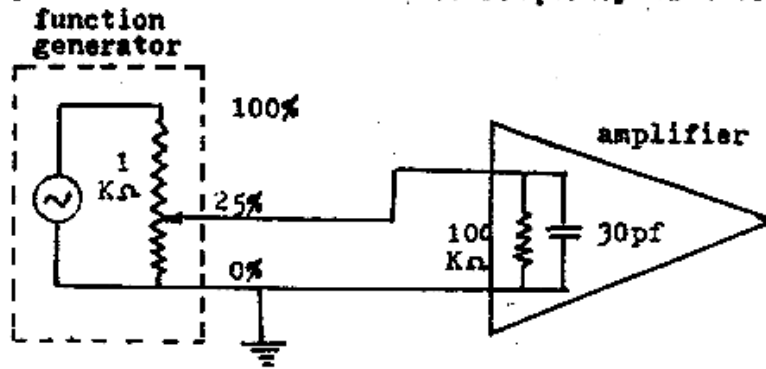
- 20% 1. A function generator uses  $1\text{ K}\Omega$  potentiometer to adjust the signal amplitude. The input impedance of the amplifier is  $100\text{ K}\Omega$  paralalled with  $30\text{ pf}$ . If the slider is on the 10% and 25% of the potentiometer, how many times the minimum cut-off frequency will be? ( 20% )



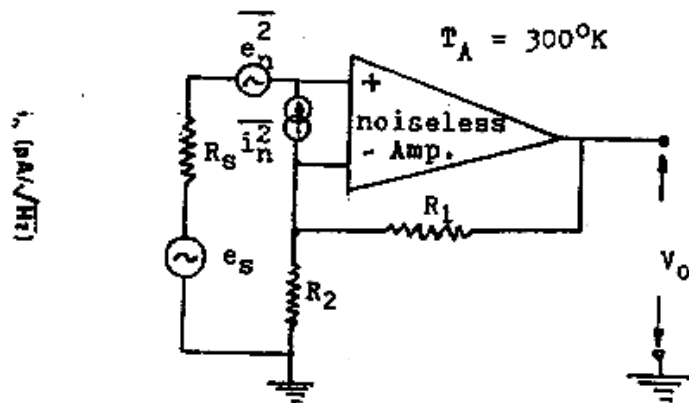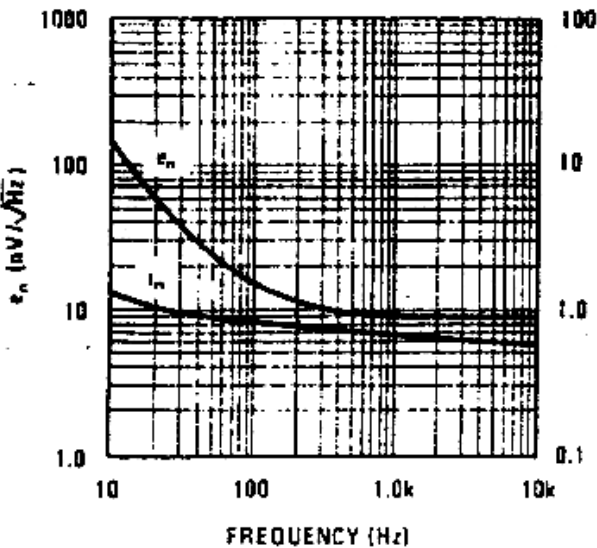- 20% 2. Determine the total equivalent input noise per unit bandwidth for the amplifier as shown. If the amplifier is operate at 2 KHz from a source resistance of  $1\text{ K}\Omega$ ,  $R_1$  and  $R_2$  are  $200\text{ K}\Omega$  and  $1\text{ K}\Omega$  respectively. ( Boltzmann's Constant =  $1.38 \times 10^{-23}\text{ w-sec / }^\circ\text{K}$  ) ( 20% )



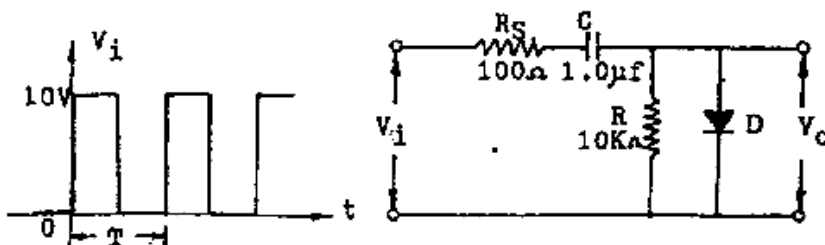- 20% 3. In the circuit as shown, at  $t = 0$  there is applied a symmetrical square-wave signal of amplitude  $10\text{ V}$  and frequency  $5\text{ KHz}$ . Draw the first several cycles of the output waveform, assuming that the capacitor is initially uncharged. ( 20% )




# 國立中央大學八十四學年度碩士班研究生入學試題卷

所別: 光電科學研究所

組 科目: 電子學

共 2 頁 第 2 頁

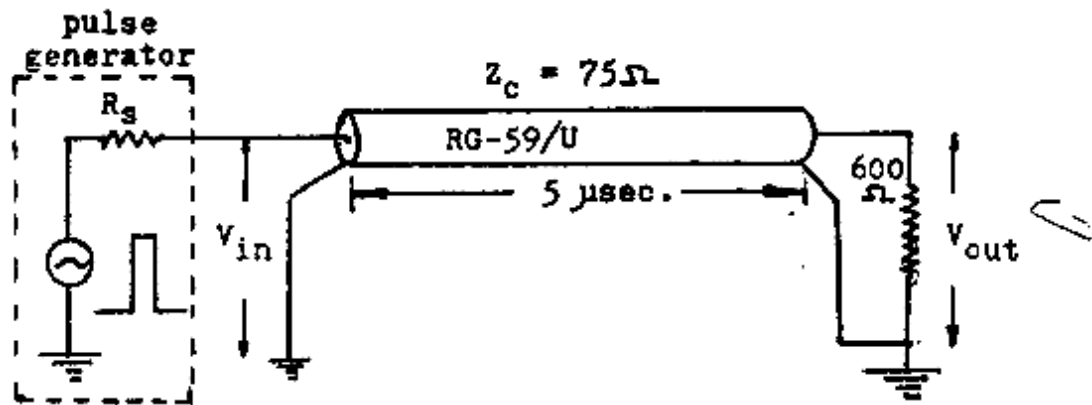4. A pulse generator whose impedance is  $R_s = 45\Omega$  delivers a 2- $\mu\text{sec}$  8-V pulse to a lossless RG-59/U ( $Z_c = 75\Omega$ ) coaxial cable and terminated in  $600\Omega$ . The one-way delay of the cable is 5  $\mu\text{sec}$ . Find the voltage waveforms at the input and output of the cable. (20%)



5. The four-diode gate is shown, if  $R_c = R_L = 100\text{K}\Omega$ ,  $V_I = 0$ ,  $R_f = 25\Omega$ ,  $R_R = \infty$ ,  $R = 100\Omega$  (set at its midpoint), if  $V_s = 2 V_{\text{peak}}$  compute A,  $(V_n)_{\text{min}}$ ,  $(V_c)_{\text{min}}$ . (20%)

