

系所別: 電機工程學系 甲組 科目: 電子學

乙.丙組

通訊工程學系 丙組

參考用

1. 選擇題(15分, 答錯每小題倒扣2分)

For the circuit shown in Fig. 1.1, let  $R_1 + R_2 = 100\text{ k}\Omega$ ,  $R_D = 4\text{ k}\Omega$ ,  $R_S = 1\text{ k}\Omega$ ,  $\mu_n C_{ox} = 100\text{ }\mu\text{A/V}^2$ ,  $(W/L)_n = 2.5\text{ }\mu\text{m}/1\text{ }\mu\text{m}$ ,  $V_T = 1\text{ V}$ , and  $V_A = \infty$ . There are five bias conditions available: (A)  $R_1/R_2 = 10$ , (B)  $R_1/R_2 = 5$ , (C)  $R_1/R_2 = 2$ , (D)  $R_1/R_2 = 1$ , and (E)  $R_1/R_2 = 0.1$ .

- (1) Which condition could provide the maximum voltage gain  $v_o/v_i$ ? (5分)
- (2) Which condition could provide the maximum output symmetrical signal swing? (5分)
- (3) Which condition could cause the minimum dc power dissipation in the MOS transistor? (5分)

 


Fig. 1.1

 


Fig. 2(a)

 


Fig. 2(b)

 


Fig. 2(c)

2. 選擇題(15分)

Consider the circuits (a), (b), and (c) shown in Fig.2, assume that every transistor is biased in the forward-active mode and has the same  $\beta_F = 100$ ,  $V_{BE(on)} = 0.7\text{ V}$ , and  $V_A = \infty$ . If the current sources  $I_C$ ,  $I_{E_0}$ , and  $I_{E_1}$  are adjusted such that each  $Q_1$  transistor has the same dc collector current and hence, the same small-signal parameters.

- (1) Consider the voltage gain  $A_v = v_o/v_i$ , (A)  $A_{va} > A_{vb} > A_{vc}$  (B)  $A_{vb} > A_{vc} > A_{va}$  (C)  $A_{va} = A_{vb} > A_{vc}$  (D)  $A_{vb} > A_{va} > A_{vc}$  (E)  $A_{vb} > A_{va} = A_{vc}$ . (10分, 答錯倒扣4分)
- (2) Consider the input resistance  $R_i$ , (A)  $R_{ia} > R_{ib} > R_{ic}$  (B)  $R_{ib} > R_{ic} > R_{ia}$  (C)  $R_{ia} = R_{ib} > R_{ic}$  (D)  $R_{ib} > R_{ia} > R_{ic}$  (E)  $R_{ib} > R_{ia} = R_{ic}$ . (5分, 答錯倒扣2分)

3. (20分)

As shown in Fig. 3, assuming all transistors to be identical with  $\beta$  infinite,  $\alpha = 1$  and keeping the current in each junction the same.

- (1) Derive an expression for the output current  $I_o$  in terms of  $V_{CC}$ ,  $V_{BE}$ ,  $R_1$ ,  $R_2$  and  $R_E$ . (10分)
- (2) What will be the relationship of  $R_1$ ,  $R_2$  and  $R_E$ , which keeps output current  $I_o$  independent of  $V_{BE}$ ? (5分)
- (3) For  $V_{CC} = 15\text{ Volts}$ , and  $V_{BE} = 0.7\text{ Volts}$ , design the circuit to obtain an output current of  $1\text{ mA}$ .

What is the lowest allowable voltage at the collector of  $Q_3$ ? (5分)

 


Fig. 3

注意: 背面有試題

系所別: 電機工程學系 甲組 科目: 電子學

2. 丙組

通訊工程學系 丙組

4. (20 分)

For the amplifier as shown in Fig. 4, assuming that  $V_s$  has a zero dc component,

- (1) Find the dc voltages  $V_{B1}$ ,  $V_{B2}$ ,  $V_{E2}$ ,  $V_O$  and the dc emitter current  $I_{E2}$ . Let the BJTs have  $\beta = 100$  and neglect  $I_{B2}$ . (10 分)
- (2) Use feedback analysis to find the values of  $V_O/V_s$  and  $R_{in}$ . (10 分)

 


Fig. 4

5. (15 分)

In the shown circuit (Fig. 5), the internally compensated OP amp has high-order poles remote from its unity-gain frequency  $f_u$ , a relatively large open-loop gain  $A_O$ , and otherwise ideal characteristics.

- (a) Find expression for the loop gain. (4 分)
- (b) Find expressions for the potential conditions for oscillation. (8 分)
- (c) Estimate the required value of  $R_2/R_1$ , if the angular frequency of oscillation is equal to  $2/RC$ . (3 分)

 


Fig. 5

6. (15 分)

For the shown one-transistor DRAM cell,

- (a) if  $C_S = 20$  fF, bit-line capacitance  $C_B = 1$  pF,  $V_{DD} = 3.3$  V, and NMOS transistor has a  $V_t$  (including the body effect) = 0.8 V, estimate the output readout voltage, i.e. change in the voltage on the bit line resulting from connecting a  $C_S$  to it, for a stored 1 and a stored 0, assuming the bit lines are precharged to  $V_{DD}/2$  in a read operation. (10 分)
- (b) if  $C_S = 15$  fF, refresh is required within 5 ms, and a signal loss on the  $C_S$  of 0.3 V can be tolerated, estimate the largest acceptable leakage current present at the cell. (5 分)

 


Fig. 6

參考用