

國立中央大學通訊工程學系 104 學年度碩士在職專班入學筆試


【電子學】試卷

考試地點：通訊館一樓 E1-109 室


考試時間：100 分鐘

試題總分：100 分

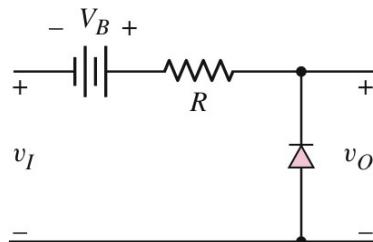1. (20%) Let the diode cut-in voltage be V_γ . If the input voltage v_I is a sine function, plot the steady-state output waveforms v_O in the following circuits.




(a)

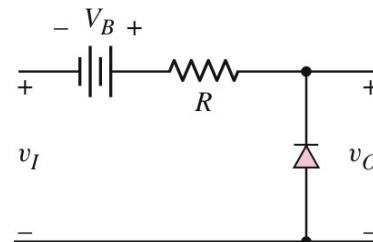


(b)

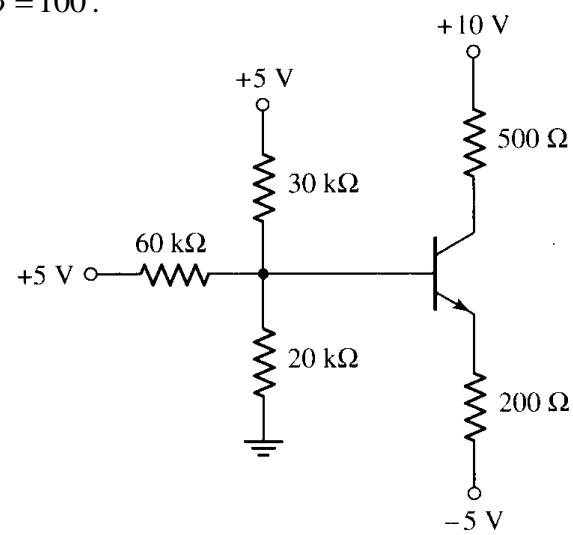2. (25%) Find I_{CQ} and V_{CEQ} of the transistor, assuming $\beta = 100$.



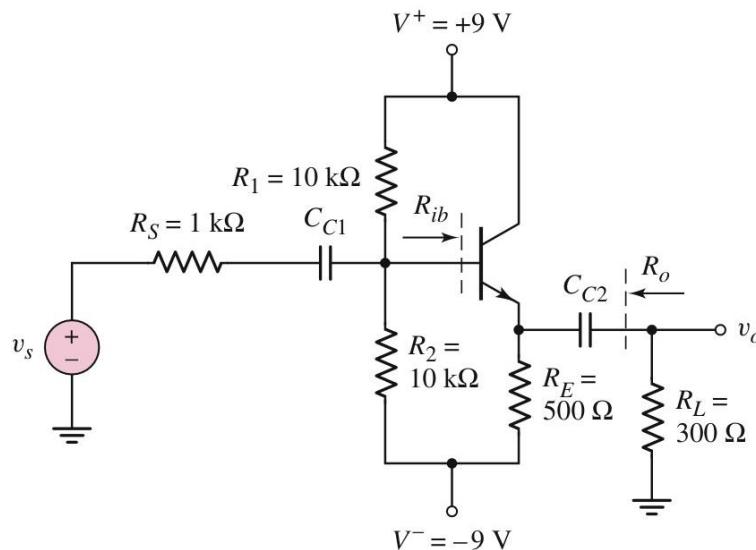3. (30%) The transistor parameters are $\beta = 180$ and $V_A = \infty$.

- Find I_{CQ} and V_{CEQ} . (10 points)
- Find the small-signal voltage gain $A_v = v_o / v_s$. (10 points)
- Determine the input and output resistances R_{ib} and R_o . (10 points)



背面尚有試題

國立中央大學通訊工程學系 104 學年度碩士在職專班入學筆試
 【電子學】試卷

考試地點：通訊館一樓 E1-109 室 考試時間：100 分鐘 試題總分：100 分

4. (25%) Assume that all transistors are matched. Let

$$I_{REF} = 0.2mA, K_n = 0.2mA/V^2, V_{TN} = 1V, \text{ and } \lambda = 0.02V^{-1}.$$

Determine the output resistance looking into the drain of M_6 .

