

國立中央大學 110 學年度碩士班考試入學試題

所別： 電機工程學系 碩士班 固態組(一般生)
電機工程學系 碩士班 系統與生醫組(一般生)
電機工程學系 碩士班 電波組(一般生)

共 3 頁 第 1 頁


科目： 電子學

本科考試禁用計算器

*請在答案卷(卡)內作答


1. 計算題(10分)

Figure P1 shows the BJT amplifier with a current gain β of BJT is 100, thermal voltage $V_T = 25$ mV and collector current $I_C = I_S \exp(V_{EB} / V_T)$. Assume that when V_{EB} is 0.7 V, I_C is 1 mA. When V_C is -5 V, design R_E and R_C to make I_C equal to 4 mA. Note the answer must be rounded to two decimal places. (R_E 與 R_C 各 5 分。)

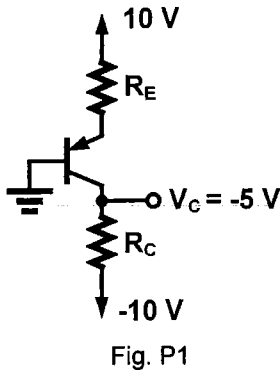


2. 計算題(10分)

Figure P2 shows a BJT amplifier with infinite current gain β . Assume the threshold voltage V_D of ideal diode is 0.7 V and ignore the base current of BJT. Find out the operation region of transistor Q_1 and Q_2 (active or saturation region). (全對 10 分，部分對 3 分，全錯 0 分。)

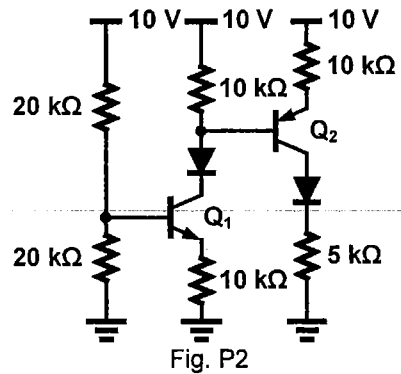

3. 計算題(10分)

Figure P3 shows a common-source amplifier which is biased at saturation region with threshold voltage $V_{th} = 1$ V and channel-length modulation parameter $\lambda = 0.01$ V^{-1} . Find the small signal voltage gain $-g_m r_o$.

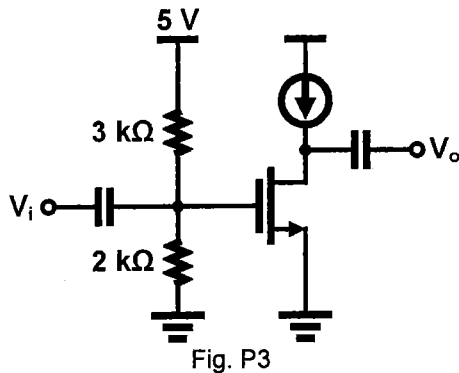


4. 計算題(10分)

The ideal OP amplifier circuit is shown in Fig. P4.

4-1 (5分) If differential gain $A_d = \infty$, find out V_o .

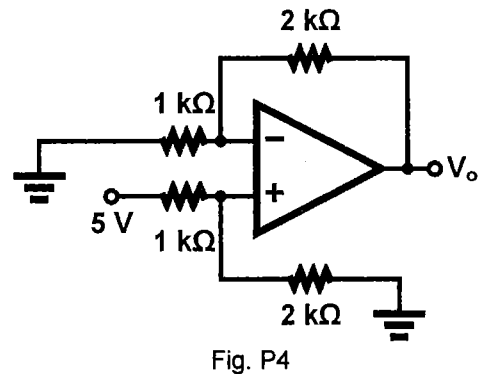4-2 (5分) If differential gain $A_d = 50$ V/V, find out V_o .



注意:背面有試題

國立中央大學 110 學年度碩士班考試入學試題

所別： 電機工程學系 碩士班 固態組(一般生)
電機工程學系 碩士班 系統與生醫組(一般生)
電機工程學系 碩士班 電波組(一般生)

共 3 頁 第 2 頁

科目： 電子學

本科考試禁用計算器

*請在答案卷(卡)內作答

5. 計算題(10 分)

Figure P5 shows a possible realization of the folded cascode amplifier. All the MOSFETs have $|V_A| = 5 \text{ V}$. Let $I = 100 \mu\text{A}$, and assume that the MOSFETs are operating at $V_{OV} = 0.2 \text{ V}$. Assume the current sources are ideal. Please determine

5-1 (5 分) the output resistance R_{out} .

5-2 (5 分) the voltage gain A_V .

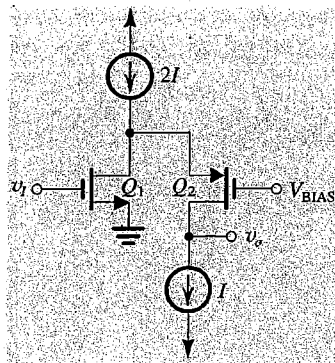


Fig. P5

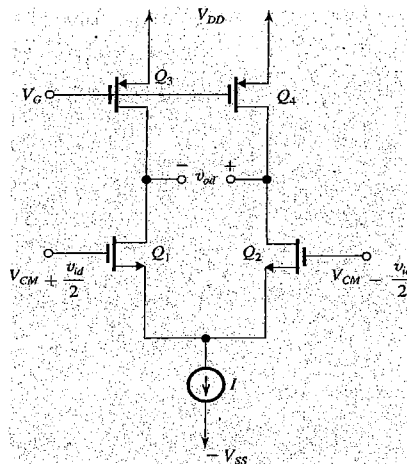


Fig. P6

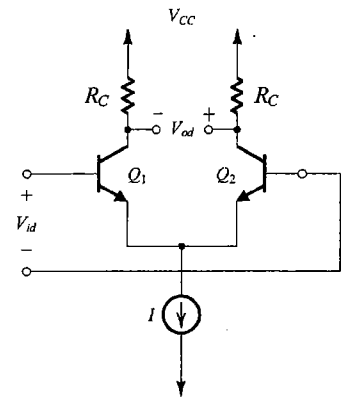


Fig. P7

6. 計算題(10 分)

The differential amplifier of figure P6 is fabricated in a $0.18\text{-}\mu\text{m}$ CMOS technology for which $\mu_n C_{ox} = 4\mu_p C_{ox} = 400 \mu\text{A/V}^2$, and $|V_A| = 10 \text{ V}/\mu\text{m}$. If the bias current $I = 200 \mu\text{A}$ and all transistors have a channel length twice the minimum and are operating at $|V_{OV}| = 0.2 \text{ V}$. Please find

6-1 (5 分) W/L of Q_1 and Q_2 .

6-2 (5 分) the differential voltage gain A_d .

7. 計算題(10 分)

Figure P7 shows that a bipolar differential amplifier with a bias current $I = 0.5 \text{ mA}$ utilizes transistors for which $V_A = 50 \text{ V}$ and $\beta = 100$. The collector resistances $R_C = 5 \text{ k}\Omega$ and the mismatch ΔR_C between the collector resistances is within 10%.

7-1 (5 分) Find differential voltage gain A_d .

7-2 (5 分) Find the common-mode rejection ratio (CMRR).

注意:背面有試題

國立中央大學 110 學年度碩士班考試入學試題

所別： 電機工程學系 碩士班 固態組(一般生)
電機工程學系 碩士班 系統與生醫組(一般生)
電機工程學系 碩士班 電波組(一般生)

共 3 頁 第 3 頁

科目： 電子學

本科考試禁用計算器

*請在答案卷(卡)內作答

8. 計算題(15 分)

Figure P8 shows a generalized high-frequency equivalent circuit for the common-source amplifier. For the case of $g_m = 2 \text{ mA/V}$, $C_{gs} = 20 \text{ fF}$, $C_{gd} = 5 \text{ fF}$, $C_L = 30 \text{ fF}$, $R'_{sig} = 10 \text{ k}\Omega$, and $R'_L = 20 \text{ k}\Omega$.

8-1 (5 分) Use the Miller approach to estimate the 3-dB frequency f_H .

8-2 (5 分) Use the method of open-circuit time constants to estimate the 3-dB frequency f_H .

8-3 (5 分) Also, find the frequency of the transmission zero f_Z .

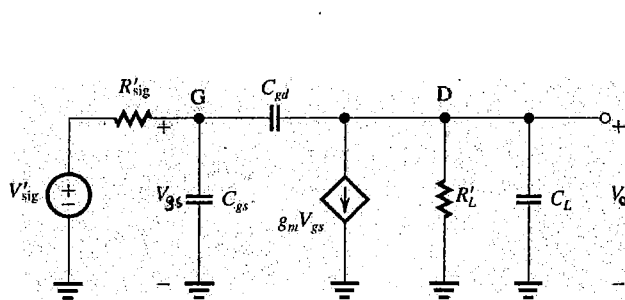


Fig. P8

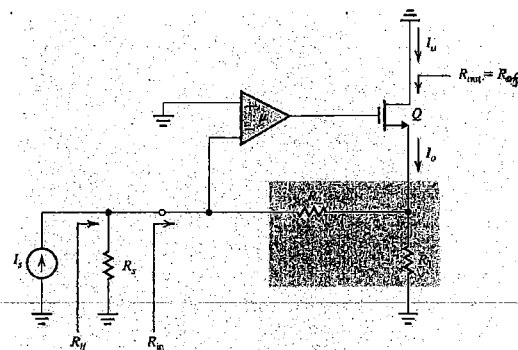


Fig. P9

9. 計算題(15 分)

Figure P9 shows a feedback current amplifier formed by cascading an inverting voltage amplifier μ with a MOSFET Q . For the case of $\mu = 100 \text{ V/V}$, $R_s = R_{id} = \infty$, $R_1 = 10 \text{ k}\Omega$, and $R_2 = 90 \text{ k}\Omega$; For Q : $g_m = 5 \text{ mA/V}$ and $r_o = 20 \text{ k}\Omega$.

9-1 (5 分) Find the value of close-loop gain $A_f = I_o/I_s$.

9-2 (5 分) Find the value of input resistance R_{in} .

9-3 (5 分) Find the value of output resistance R_{out} .