

國立中央大學 資訊工程學系
95 學年度 碩士在職專班 招生入學考試命題紙

科目： 數 位 設 計

第一頁 共 一 頁

1. Use Karnaugh map to simplify the Boolean function $F(A, B, C, D) = \Sigma m(0, 1, 4, 5, 12, 13)$ in sum-of-products form. (10%)
2. Determine the prime implicants and essential prime implicants of the following Boolean function: $F(A, B, C, D) = \Sigma m(0, 1, 4, 5, 12, 13)$. (10%)
3. Convert the function $wx'y' + yw'z' + yxz + yxw$ into 3-input NAND gates. (15%)
4. Design a 4-bit carry-look-ahead (CLA) generator. (15%)
5. Using two 4:1 multiplexers to implement a full-adder. (15%)
6. Show how to implement a D flip-flop starting with a J-K flip-flop. (15%)
7. Design a three flip-flop counter that counts in the following sequence: 0, 2, 7, 4, 6, 3, 1, and repeat. (20%)