

國立中央大學100學年度碩士班考試入學試題卷

所別：電機工程學系碩士班 固態組(一般生) 科目：工程數學 共 1 頁 第 1 頁
電機工程學系碩士班 系統與生醫組(一般生)

本科考試禁用計算器

*請在試卷答案卷(卡)內作答

1. (10%) Prove that if matrix A and matrix B are similar $n \times n$ matrices, then they have the same eigenvalues.
2. (a) (5%) Find the least squares solution of the following system $Ax=b$.
(b) (5%) Find the orthogonal projection of b onto the column space of A .

For the above questions, where $A = \begin{bmatrix} 0 & 2 \\ 3 & 0 \\ 1 & 0 \end{bmatrix}$, $b = \begin{bmatrix} 1 \\ 1 \\ 3 \end{bmatrix}$.

3. (a) (5%) Find the determinant of the matrix A by using cofactors method.
(b) (5%) Show the sum of all eigenvalues of A .

For the above questions, where $A = \begin{bmatrix} 2 & 0 & 0 & 0 \\ 4 & -2 & 0 & 0 \\ -5 & 6 & 1 & 0 \\ 1 & 5 & 3 & 3 \end{bmatrix}$.

4. (15%) Solve the following initial value problem.
 $y'' + 2ty' - 4y = 1$, $y(0) = y'(0) = 0$
5. (15%) Find the inverse Laplace transform of the following function.

$$F(s) = \frac{s^3}{s^4 + 4a^4}$$

6. (10%) For two continuous-time periodic signals $x(t) = e^{-2t}$, for $0 \leq t \leq T$ and $h(t) = e^{j2\pi k_0 t/T}$, both the signals $x(t)$ and $h(t)$ have the same repetition period $T=2$ and k_0 belongs to an integer. Please find the Fourier series coefficients for $y(t) = x(t)h(t)$ in terms of k_0 .

7. (15%) Show that if $v(x, y)$ is a harmonic conjugate of $u(x, y)$, then their product uv is also harmonic.

8. (15%) Evaluate the integral $\int_0^{2\pi} \frac{\cos^2 \theta}{5 - 4 \cos \theta} d\theta$.

參考用

所別：電機工程學系碩士班 固態組(一般生)
 電機工程學系碩士班 系統與生醫組(一般生)
 電機工程學系碩士班 電波組(一般生)

科目：電子學

共 2 頁 第 / 頁

本科考試禁用計算器

*請在試卷答案卷(卡)內作答

1 問答題 (21 分)

1-1 Consider the BJT circuits in Fig. 1, please specify the corresponding configuration for each circuit (common-emitter, common-base, or emitter-follower?) (6 分)

1-2 Which of the following statements are true? (15 分)

- (a) Fig. 1.1 A amplifier has a voltage gain $|A_v| > 1$,
- (b) Fig. 1.1 B amplifier has a current gain $|A_i| > 1$,
- (c) Fig. 1.1 C amplifier has a voltage gain $|A_v| < 1$.
- (d) Fig. 1.1 B amplifier has the highest R_{in} ,
- (e) Fig. 1.1 amplifier C has the lowest R_o .

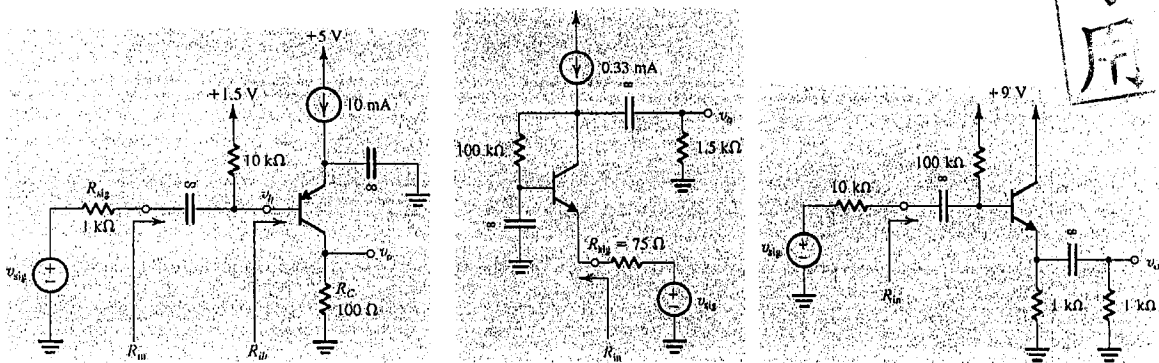


Fig. 1.1 (A)

(B)

(C)

2. 計算題 (16 分)

For the circuits in Fig. 2, $\mu_n C_{ox} = 2.5 \mu_p C_{ox} = 20 \mu A/V^2$, $|V_{TH}| = 1 V$, $\lambda = 0$ (or $V_A = \infty$), and $L = 1 \mu m$ and $W = 4 \mu m$ for all MOSFETs. Find the labeled currents and voltages, I_1 , V_2 , I_3 , and V_4 .

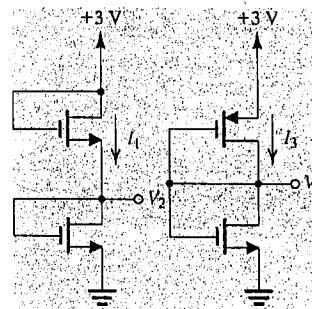


Fig. 2

(a)

(b)

3. 計算題與問答題 (16 分)

A second-order filter is shown in Fig. 3.

3-1 Please derive the transfer function $T(s) = V_o(s) / V_i(s)$ in terms of R , L , and C . (12 分)

3-2 What is the filter type of this circuit? (4 分)

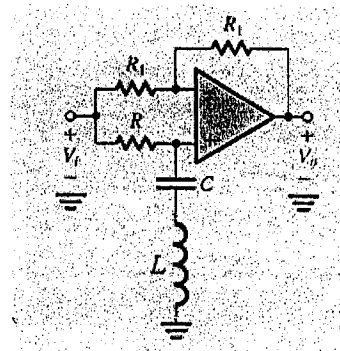


Fig. 3

注意：背面有試題