

所別：光電科學與工程學系碩士班 不分組(一般生) 科目：電子學 共 2 頁 第 1 頁
 光電科學與工程學系碩士班 不分組(在職生)

本科考試可使用計算器，廠牌、功能不拘

*請在試卷答案卷(卡)內作答

1. Figure 1 shows an op-amp circuit for 4-bit digital-to-analog converter (DAQ), which can convert a 4-bit digital word $a_3a_2a_1a_0$ to an analog output. The value of each bit is represented by a corresponding switch. That is, if a_0 is 1 then switch S_0 connects to the +5-V power supply, while if a_0 is 0 then switch S_0 connects to ground.
- (a) Find R_1 and R_2 so that $v_o = -\frac{R_3}{8}(2^0 a_0 + 2^1 a_1 + 2^2 a_2 + 2^3 a_3)$. (10%)
- (b) Find R_3 so that v_o ranges from 0 to -24 volts. That is, the digital words 0000 and 1111 are converted to 0 V and -24 V, respectively. (5%)
- (c) Based on this circuit, please design an op-amp circuit which can convert a 4-bit digital word to an analog output ranging from 0 to 12 V. Any reasonable scheme is allowed. (10%)

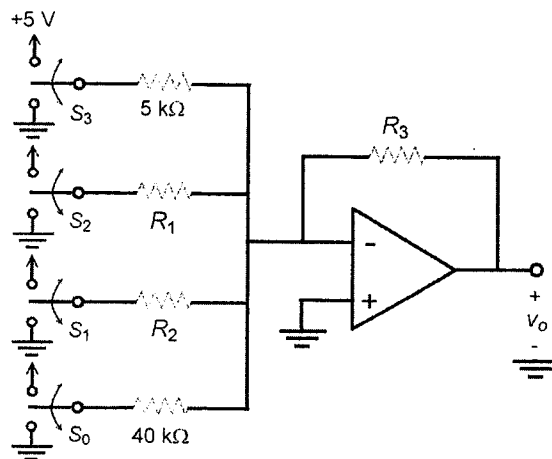


Fig. 1

2. For an active filter shown in Figure 2, please answer the following questions:
- (a) Determine the transfer function $H(s) = V_o/V_s$, where $s = j\omega$. (5%)
- (b) Show that this active filter is a band-pass filter. (3%)
- (c) For $R_1 = 1 \text{ k}\Omega$ and $C_2 = 0.1 \text{ }\mu\text{F}$, find R_2 and C_1 so that the band-pass filter has a resonant frequency at 500 rad/s. (6%)
- (d) Draw the Bode plot for the magnitude of the band-pass filter in (c). (5%)
- (e) For the band-pass filter in (c), find the bandwidth B and quality factor Q . (6%)

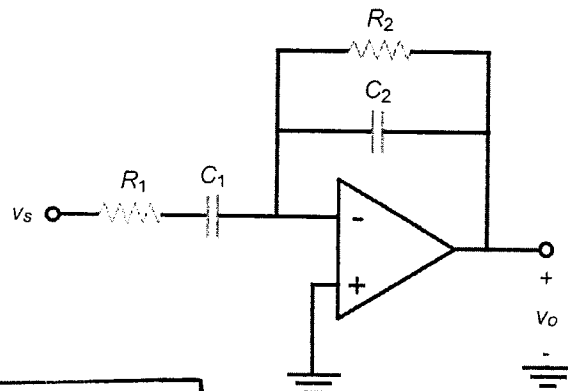


Fig. 2

注意：背面有試題

3. The cut-in voltage for each diode in Fig. 3 is $V_T = 0.5$ V.
- Find V_1 and V_2 and each diode current for $R_1 = 2$ K Ω , $R_2 = 3$ K Ω , and $R_3 = 2$ K Ω . (5%)
 - Define the load line of diode D_3 in this circuit. (5%)

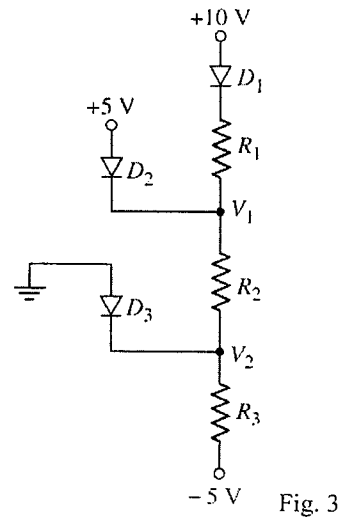


Fig. 3

4. For the circuit in Figure 4, the parameters are $V_{TN} = 1.5$ V and $K_n = 0.6$ mA/V² for transistors M_1 and M_2 .
- Determine that I_D , V_{GS1} , V_{DS1} , V_{GS2} , and V_{DS2} for transistors M_1 and M_2 , respectively. (5%)
 - Define the load lines for transistor M_1 . (5%)
 - Sketch the current-voltage characteristics of transistors M_1 and M_2 . (10%)

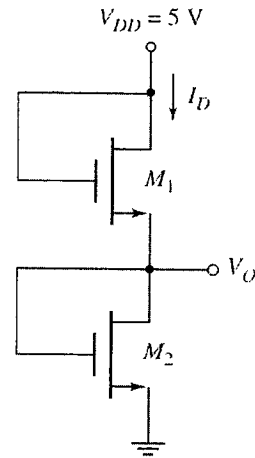


Fig. 4

5. A common-gate circuit shown in Figure 5. The transistor parameters are $V_{TN} = 0.5$ V, $K_n = 2$ mA/V², and $\lambda = 0$, $C_{gs} = 10$ pF, $C_{gd} = 2$ pF.
- Determine the upper 3 dB frequency. (10%)
 - Determine the midband voltage gain. (10%)

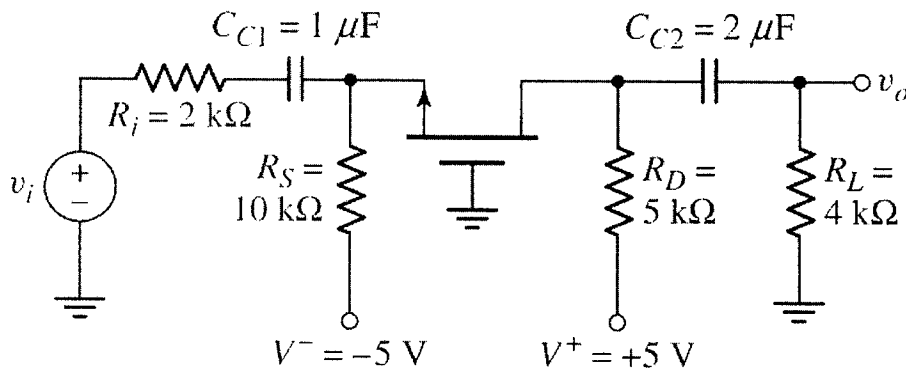


Fig. 5

注意：背面有試題