

- Q1: (a) What is the *8's complement* of an octal number 7654321 ?
 (b) What is the *7's complement* of an octal number 7654321 ?
 (c) Convert the octal number 7654321 to hexadecimal number.
 (15%)

- Q2: Use K-map method to simplify the following Boolean function in (a) sum of products and (b) product of sums.

$$F(w,x,y,z) = x'y' + x'z' + w'xy'z$$

$$d(w,x,y,z) = \Sigma(4,6,14)$$

(20%)

- Q3: (a) List the truth table of a function $F(A,B,C,D) = A \oplus B \oplus C \oplus D$ where the symbol \oplus denotes the Exclusive-OR function.

- (b) List the truth table of a function $F(A,B,C,D) = A \odot B \odot C \odot D$ where the symbol \odot denotes the Equivalence function.

(10%)

- Q4: (a) Use a *decoder* to implement the following Boolean function:

$$F(w,x,y,z) = \Sigma(0,1,2,3,4,11,12,13,14,15)$$

- (b) Use a *multiplexer* to implement the same Boolean function

(20%)

- Q5: Given you the flow table (after state reduction) as shown below.

- (a) Assign output values to the dashes associated with the unstable states.

- (b) Design the asynchronous sequential circuit without using SR latch.

- (c) Design the asynchronous sequential circuit using SR latch.

	x_1x_2			
	00	01	11	10
a	a, 0	a, 1	a, 0	b, -
b	a, -	a, -	b, 1	b, 1

(35%)