

所別：電機工程學系碩士班 甲組(一般生) 科目：電子學

(學位在職生)

1. 計算題 (20 分)

1-1 (5 分) The circuit of Fig. 1(a) is a source follower configuration with positive feedback. The transconductances of Q_1 and Q_2 are g_{m1} and g_{m2} , respectively. The capacitances C_{gs} and C_{gd} can be neglected. Also neglect output resistance r_o and body effect. Calculate the input resistance R_{in} .

1-2 (5 分) The circuit of Fig. 1(b) is a common-source with a resistive feedback which can be used as a lossy active inductor. Calculate the s-domain output resistance $Z_{out}(s)$ in terms of R_F , g_m , C_{gs} , and C_{gd} .

1-3 (10 分) The circuit of Fig. 1(c) is a gyrator which can be used as an active inductor. Assume that ideal op amps are applied in the circuit. Calculate the s-domain input impedance $Z_{in}(s)$.

 


Fig. 1(a)

 


Fig. 1(b)

 


Fig. 1(c)

2. 計算題 (15 分)

A feedback circuit is shown in Fig. 2, which consists of a common-gate amplifier formed by Q_1 and R_D . The capacitive divider C_1 , C_2 senses the output voltage, applying the result to the gate of common-source transistor Q_f . The bias circuit for Q_f is not shown. The design parameters are illustrated as follows, $g_{m1} = 5 \text{ mA/V}$, $g_{mf} = 1 \text{ mA/V}$, $R_D = 10 \text{ k}\Omega$, $C_1 = 0.9 \text{ pF}$, and $C_2 = 0.1 \text{ pF}$. Assume that C_1 and C_2 are sufficiently small that their loading effect on the basic amplifier can be neglected. Also neglect output resistance r_o and body effect.

2-1 (10 分) Derive the expressions of the transimpedance gain V_O / I_S .

2-2 (5 分) Find the output resistance R_{out} .

 


Fig. 2 Circuit for Problem 2

 


Fig. 3 Circuit for Problem 3

注意：背面有試題

所別：電機工程學系碩士班 甲組(一般生) 科目：電子學

(學位在職生)

3. 計算題 (15 分)

A CMOS active-loaded differential amplifier is shown in Fig. 3. For this process, assume that for all transistors $W/L=5.0 \mu\text{m}/0.25 \mu\text{m}$. The design parameters are listed as follows: $\mu_n C_{ox} = 250 \mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2$, $V'_{An} = 5 \text{V}/\mu\text{m}$, and $|V'_{Ap}| = 6 \text{V}/\mu\text{m}$. The bias current $I = 0.2 \text{mA}$, and bias current source has an output resistance $R_{SS} = 25 \text{k}\Omega$ and an output capacitance $C_{SS} = 0.2 \text{pF}$. And the total capacitance at the input of the current mirror is $C_m = 50 \text{fF}$. The total capacitance at the output is $C_L = 40 \text{fF}$.

3-1 (6 分) Calculate the low frequency values of differential gain A_d , and common mode gain A_{cm} .

3-2 (6 分) Derive the expressions of the high frequency differential gain $A_d(s) = V_O / V_{id}$ in terms of g_{m1} , g_{m3} , C_L , C_m , R_O (R_O is the resistance of r_{o2} and r_{o4} in parallel).

3-3 (3 分) The value of dominant pole f_{p1} .

4. 電路設計題: Static CMOS (15 分)

Design the static complementary MOS pullup and pulldown networks for these logic expressions:

4-1 (5 分) $F1 = (AB+CD)'$

4-2 (5 分) $F2 = [(A+B)C+D]'$

4-3 (5 分) For a CMOS process, assume that the mobility for MOS transistors $\mu_n = 3 \mu_p$, $|V_{tp}| = V_m$, and the minimum channel lengths for all MOS transistors are chosen. Size the width of MOS transistors in problem 4-1 such that the circuit's rise and fall times are approximately equal.

5. 電路設計題: Pseudo-nMOS and dynamic CMOS gates (10 分)

Design the circuits for pseudo-nMOS gate and dynamic CMOS gate for the function $F = [(A+B+C)D + EF]'$

6. 電路設計題: Dynamic shift register (10 分)

Memory is an important part of digital systems. It is for temporary storage of the output produced by a combinational circuit for use at a later time in the operation. The simplest memory machine we can build with the dynamic latch is a shift register.

Design a one-bit input and a one-bit output positive edge-triggered dynamic Master-slave D-type shift register. The circuits you need are two inverters and two CMOS transmission gates.

7. 簡答與說明題(15 分)

7-1 (5 分) Derive the expressions of the dynamic switching power of CMOS logic circuit. Can we reduce the power by decrease the operation frequency?

7-2 (5 分) Find the output function of Fig.7-2.

7-3 (5 分) Find the output function C_3 of Fig.7-3.

 


Fig. 7-2 Circuit for Problem 7-2

 


Fig. 7-3 Circuit for Problem 7-3