

參考用

科目：電子學(5001)

校系所組：中大光電科學與工程學系、照明與顯示科技研究所
清大電機工程學系甲組、乙組、丙組、丁組
清大光電工程研究所、電子工程研究所、
清大工程與系統科學系丁組、動力機械工程學系乙組
陽明醫學工程研究所醫學電子組

1. Consider the common-emitter amplifier circuit of Fig. 1 with a supply voltage $V_{CC} = 10V$. Assume that the BJT has $I_S = 10^{-15}A$, $\beta = 100$, $C_{\mu} = 0.2$ pF, and $C_{\pi} = 1$ pF.

 


Fig. 1

- (a) Biasing the BJT with a dc collector current $I_C = 1mA$, find dc voltage V_{BE} and R_C to provide a voltage gain $v_O / v_{bc} = -100V/V$ (5%).
- (b) Find the incremental (or small-signal) input resistance R_{in} and the input capacitance C_{in} of the amplifier. (5%)
- (c) With $R_{sig} = 1K\Omega$, find the -3dB bandwidth f_H and unity-gain bandwidth f_T of v_O / v_{sig} . (5%)

2. The parameters of the circuit shown in Fig. 2 is listed below:

$$V_{th} = 1V, \mu_n C_{ox} = 100 \mu A, \lambda = 0, \text{ and } L1 = L2 = L3 = L4 = 1\mu m$$

$$W1 = 8\mu m, W2 = W3 = W4 = 32\mu m$$

- (a) Find the voltage values at nodes V1, V2, and V3. (Neglect the body effect and channel length modulation) (15%)
- (b) What operation regions are Q1 and Q3 in (cutoff, saturation or triode)? (5%)

 


Fig. 2

注意：背面有試題

科目：電子學(5001)

參
考
用

校系所組：中大光電科學與工程學系、照明與顯示科技研究所
清大電機工程學系甲組、乙組、丙組、丁組
清大光電工程研究所、電子工程研究所、
清大工程與系統科學系丁組、動力機械工程學系乙組
陽明醫學工程研究所醫學電子組

3. Find the input impedance $Z_{in} = V/I$ of the op-amp circuit shown in Fig. 3. (15%)

 


Fig. 3

4. For the op-amp circuit shown in Fig. 4, if $v_1(0^+) = 5 \text{ V}$ and $v_2(0^+) = 0 \text{ V}$, find v_o for $t > 0$. Let $R_1 = 100 \text{ K}\Omega$, $R_2 = 200 \text{ K}\Omega$, $C_1 = 1 \mu\text{F}$, $C_2 = 0.5 \mu\text{F}$. (15%)

 


Fig. 4

注
意：背面有試題

科目：電子學(5001)



校系所組：中大光電科學與工程學系、照明與顯示科技研究所
 清大電機工程學系甲組、乙組、丙組、丁組
 清大光電工程研究所、電子工程研究所、
 清大工程與系統科學系丁組、動力機械工程學系乙組
 陽明醫學工程研究所醫學電子組

5. Fig. 5 shows a popular configuration for a two-stage CMOS OP Amp. Assuming the transconductances of $Q_1 \dots Q_8$ are $g_{m1} \dots g_{m8}$, the output resistances of $Q_1 \dots Q_8$ are $r_{o1} \dots r_{o8}$, answer the following questions to analyze its operation and design its compensation network.

 


Fig. 5

- (a) Find out the overall DC voltage gain of the CMOS OP Amp. (5%).
- (b) Assume that the load capacitance C_L and C_C are much greater than the transistor capacitances. Then we can find the CMOS OP Amp to have two poles ω_{P1} , ω_{P2} and one zero ω_Z such as:

$$\omega_{P1} \cong \frac{1}{G_{m2} R_1 R_2 C_C} \quad \omega_{P2} \cong \frac{G_{m2}}{C_L} \quad \omega_Z = \frac{G_{m2}}{C_C}$$

where G_{m2} is the transconductance of the second stage, R_1 is the output resistance of the first stage, R_2 is the output resistance of the second stage. If we already know the unity gain frequency f_t , what is the phase margin of the Op Amp in terms of f_t, f_{P2}, f_Z . (5%)

- (c) The additional phase lag provided by the zero is unwanted. A simple and elegant solution is to include a resistance R in series with C_C , as shown in Fig. 5. If we want to place the zero at infinite frequency, how should we pick the value of resistance R_∞ ? (5%)
- (d) Suppose student A selects $R = R_A > R_\infty$ and gets phase margin PM_A , student B selects $R = R_B < R_\infty$ and gets phase margin PM_B , student C selects $R = R_\infty$ and gets phase margin PM_C . Please compare their phase margins. (5%)

注意：背面有試題

科目：電子學(5001)

參考用

校系所組：中大光電科學與工程學系、照明與顯示科技研究所

清大電機工程學系甲組、乙組、丙組、丁組

清大光電工程研究所、電子工程研究所、

清大工程與系統科學系丁組、動力機械工程學系乙組

陽明醫學工程研究所醫學電子組

6. The circuit shown in Fig. 6 (a) can be used as a memory element. The output voltage with only two possible states L^+ and L^- is determined by the previous value of the trigger signal V_{in} , where $R_1 = 2\text{ k}\Omega$ and $R_2 = 10\text{ k}\Omega$:

- (a) Assuming $L^+ = 12\text{ V}$ and $L^- = -12\text{ V}$, determine the input threshold voltages V_{TH} and V_{TL} when the output state changes. (5%)
- (b) By adding R_3 ($2\text{ k}\Omega$) and V_{ref} (12 V), the circuit shown in Fig. 6 (b) becomes a comparator with hysteresis characteristics. Determine the threshold voltage V_{TH} and V_{TL} , and plot the transfer characteristic V_{in}/V_{out} of the circuit. (10%)

 


Fig. 6