

國立中央大學98學年度碩士班考試入學試題卷

所別：光電科學與工程學系碩士班 一般生 科目：電子學 共 4 頁 第 1 頁

*請在試卷答案卷(卡)內作答

1. At room temperature $V_T = 0.026$ V, consider the circuit shown in Fig. 1.
 - (a) (5%) Determine the diode current I_D and diode voltage V_D for $V_\gamma = 0.6$ V.
 - (b) (5%) Define a load line of this circuit.
 - (c) (5%) Determine the diode small-signal incremental resistance r_d .

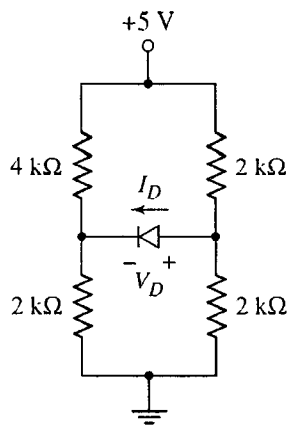


Fig. 1

2. At room temperature $V_T = 0.026$ V, consider the circuit shown in Fig. 2. The parameters are $\beta = 150$, $V_{BE(on)} = 0.7$ V, $V_A = \infty$, $C_\pi = 10$ pF, and $C_\mu = 1$ pF.
 - (a) (5%) Find the working point of transistor.
 - (b) (5%) Find the input resistance R_i .
 - (c) (5%) Determine the upper 3 dB frequencies corresponding to the input and output portions of the equivalent circuit.
 - (d) (5%) Calculate the small-signal midband voltage gain.

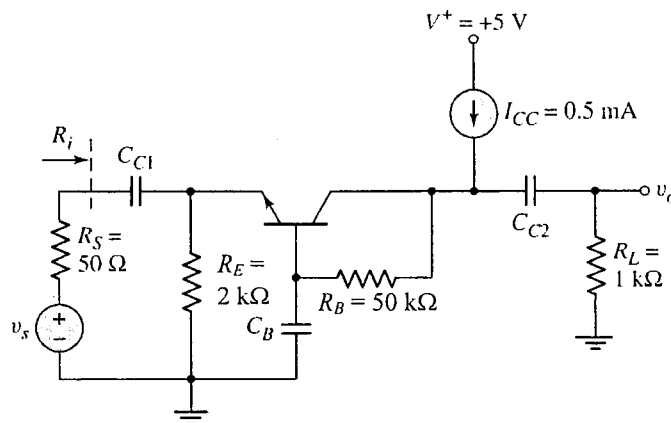


Fig. 2

參考用

注意：背面有試題

國立中央大學98學年度碩士班考試入學試題卷

所別：光電科學與工程學系碩士班 一般生 科目：電子學 共 4 頁 第 2 頁

*請在試卷答案卷(卡)內作答

3. The transistor in the circuit in Fig. 3 has parameters $V_{TN} = 0.8 \text{ V}$ and $K_n = 0.25 \text{ mA/V}^2$; $V_{DD} = 3 \text{ V}$ and $R_D = 0.5 \text{ k}\Omega$.
- (5%) Sketch the load line and plot the Q -point (working point). Please judge what is the operating bias region for each condition?
 - (5%) Determine the small-signal voltage gain A_v .
 - (5%) Please explain the reason whether the transistor in the circuit could be used as an amplifier or not.


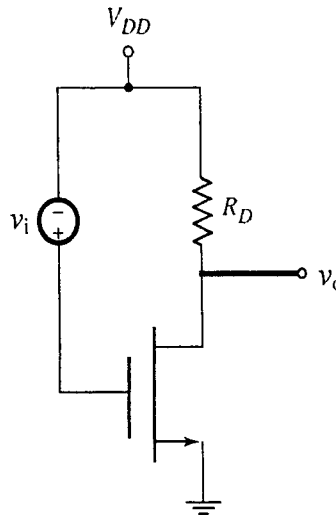


Fig. 3

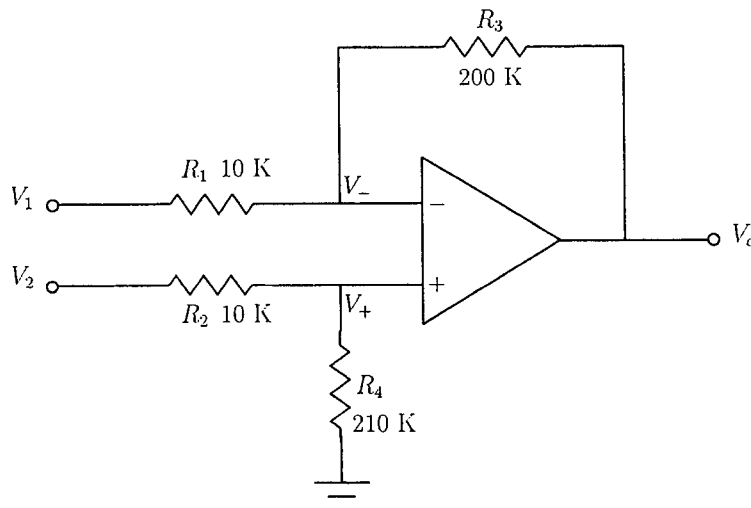4. The OP amp shown below is ideal. Determine the numerical values for the questions below.



- (4%) $V_o = \text{_____} V_2 + \text{_____} V_1$
- (2%) Find the input resistance seen by an input signal source applied at V_1 when V_2 is grounded, $R_{in,1} = \text{_____}$.
- (4%) Find the common mode input resistance for this amplifier, $R_{in,CM} = \text{_____}$.

參考用


注意：背面有試題

國立中央大學98學年度碩士班考試入學試題卷


所別：光電科學與工程學系碩士班 一般生 科目：電子學 共 4 頁 第 3 頁

*請在試卷答案卷(卡)內作答

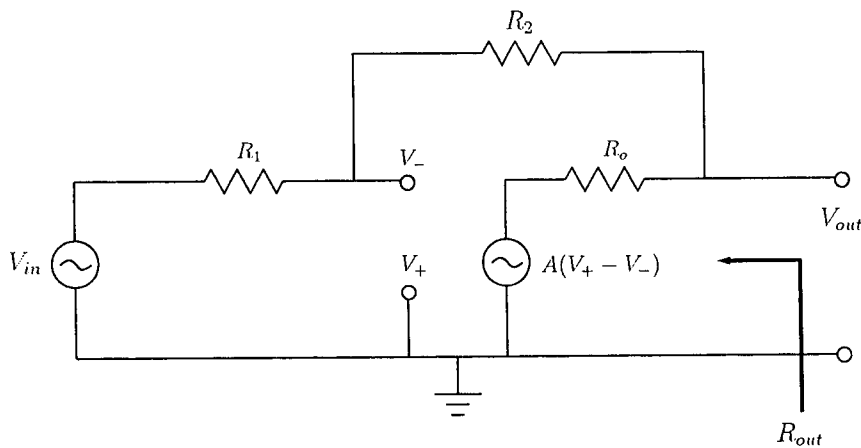5. Consider the following amplifier equivalent circuit using a non-ideal OP amp. The OP amp has a finite output resistance R_o and a finite open-loop gain A . The inverting and non-inverting terminals of the OP amp are the V_- and V_+ nodes respectively, and the output terminal is the V_{out} node. All node voltages are referenced to ground.



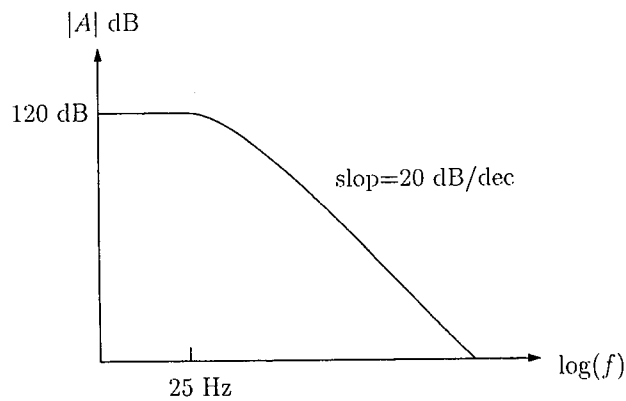- (a) (5%) Find the closed-loop gain $A_v = V_{out}/V_{in}$ in terms of R_1 , R_2 , R_o , and A .
- (b) (5%) Find the output impedance R_{out} in terms of R_1 , R_2 , R_o , and A .
- (c) (5%) The amplitude response of the open-loop gain is shown below. Compute the closed-loop voltage gain and output impedance at $f = 1$ MHz.



參考用


注意：背面有試題

國立中央大學98學年度碩士班考試入學試題卷

所別：光電科學與工程學系碩士班 一般生 科目：電子學 共 4 頁 第 4 頁

*請在試卷答案卷(卡)內作答

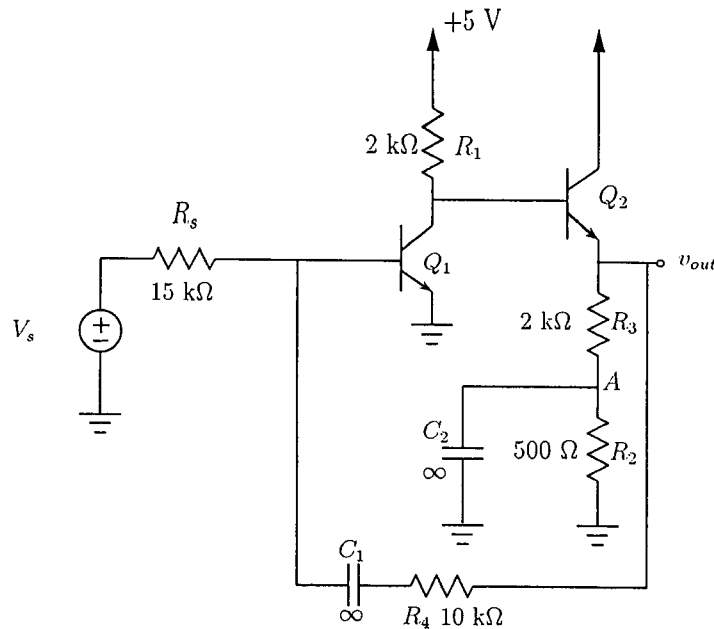6. Consider the circuit shown below. The transistor Q_1 and Q_2 are identical with $\beta = 100$ and $V_{BE} = 0.7$ V. Assume the threshold voltage $V_{th} = 26$ mV.



- If the voltage at node A is 0.5 V, what are the DC bias points (I_C , V_{CE}) for Q_1 and Q_2 ?
 - (2%) $I_{C1} = \underline{\hspace{2cm}}$ mA,
 - (2%) $V_{CE,1} = \underline{\hspace{2cm}}$ V,
 - (1%) $I_{C2} = \underline{\hspace{2cm}}$ mA,
 - (1%) $V_{CE,2} = \underline{\hspace{2cm}}$ V.
- Determine the small-signal input resistance for Q_1 and Q_2 :
 - (2%) $r_{\pi 1} = \underline{\hspace{2cm}}$ Ω ,
 - (2%) $r_{\pi 2} = \underline{\hspace{2cm}}$ Ω .
- (2%) If we consider v_{out} as the output, please specify the type of feedback topology of this circuit.
- (1%, True or False) This feedback operates at DC. Please explain your answer.
- (6%) Find the open-loop gain $A = \underline{\hspace{2cm}}$.
- (3%) Find the loop-gain $A\beta = \underline{\hspace{2cm}}$.
- (3%) What is the closed-loop gain of this circuit?

參
考
用

注：背面有試題