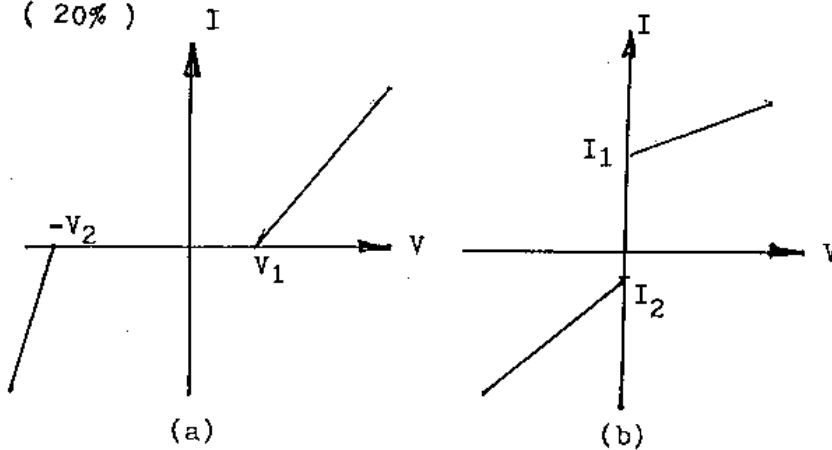


# 國立中央大學八十五學年度碩士班研究生入學試題卷


所別: 光電科學研究所    不分組    科目: 電子學    共 2 頁 第 1 頁

1. Construct circuits use ideal diodes which exhibit terminal characteristics as shown. ( 20% )




ideal diode  
 $V_F = 0, R_F = 0.$   
 $V_R = \infty, R_R = \infty.$

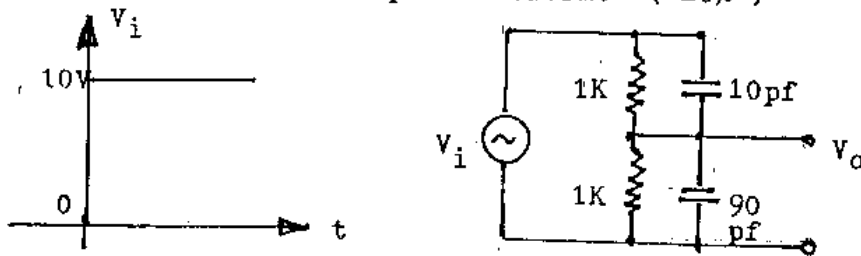2. Use the voltage - divider rule to find the output voltage  $V_o$ . If  $V_i$  is step input. Calculate and sketch the output waveform. ( 20% )




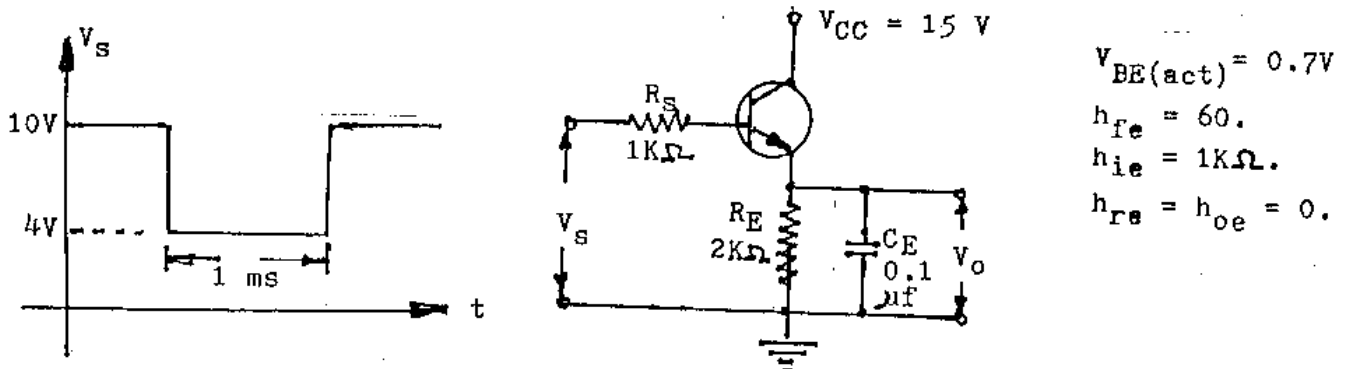3. In the circuit as shown. Assume the input pulse is wide enough to allow completion of the circuit response to the leading edge of the pulse. Find the output waveform. ( 20% )



$V_{BE(\text{act})} = 0.7\text{V}$   
 $h_{fe} = 60.$   
 $h_{ie} = 1K\Omega.$   
 $h_{re} = h_{oe} = 0.$

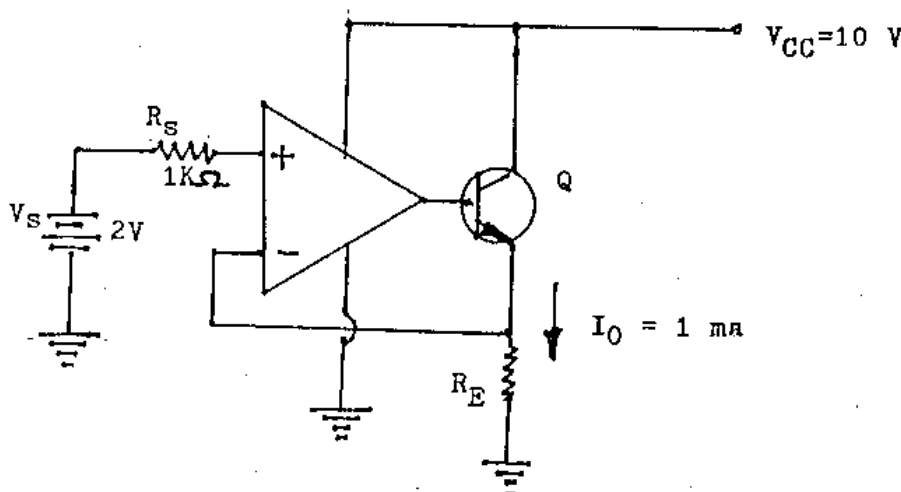4. A Circuit for a voltage-controlled current source as shown. To find the value of  $R_E$  to obtain a circuit transconductance of  $1\text{ mA/V}$ . ( 20% )



光電科學研究所  
 光電科學研究所  
 光電科學研究所

國立中央大學八十五學年度碩士班研究生入學試題卷

所別: 光電科學研究所 不分組 科目: 電子學

共 2 頁 第 2 頁

5. An astable Multivibrator using the 555 IC. If  $C=1000\text{pf}$ , and find the values of  $R_A$  and  $R_B$  that result in an oscillation frequency of 100 KHz and duty cycle of 65%.  
( 20% )

