

所別：電機工程學系碩士班 甲組(一般生) 科目：電子學  
甲組(學位在職生)

1. 計算題 (18 分)

Calculate the voltage gains ( $v_o/v_i$ ) for the following circuits:

- 1-1 Figure 1(a) shows a folded MOS amplifier formed by cascading two common source stages. Assuming  $Q_1$  and  $Q_2$  have the same transconductances of  $1 \text{ mA/V}$ , bias current  $I = 100 \mu\text{A}$ ,  $V_{A_n} = |V_{A_p}| = 2 \text{ V}$ , and the biasing current sources have an output resistance equal to that of  $Q_1$ . Find its overall voltage gain. (6 分)
- 1-2 The MOSFETs in the circuit of Fig. 1(b) are matched, having  $\mu_n C_{ox} (W/L)_1 = \mu_p C_{ox} (W/L)_2 = 1.0 \text{ mA/V}^2$ , threshold voltage  $|V_t| = 0.5 \text{ V}$ ,  $r_o = \infty$ , and feedback resistor  $R_F = 100 \text{ k}\Omega$ . Find the overall voltage gain of the amplifier. (6 分)
- 1-3 Figure 1(c) shows a circuit for a voltage to current converter employing an op-amp with an open circuit voltage gain  $A = 1000$ . The MOSFET  $Q_1$  has a transconductance  $g_m = 1.0 \text{ mA/V}$ , a source resistor  $R_S = 1 \text{ k}\Omega$ , a drain resistor  $R_D = 10 \text{ k}\Omega$  and  $r_o = \infty$ . Find its closed-loop voltage gain. (6 分)

 


Fig. 1(a)

 


Fig. 1(b)

 


Fig. 1(c)

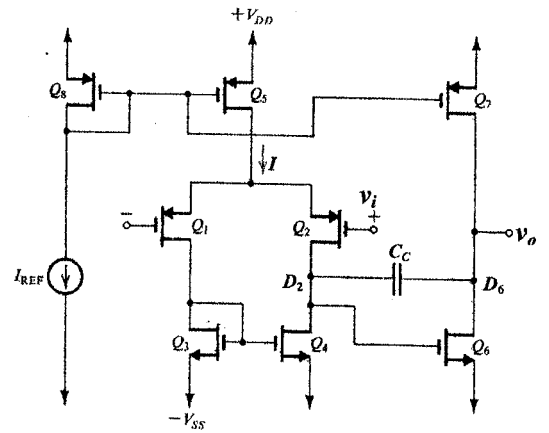


Fig. 2

2. 計算題 (18 分)

Figure 2 shows the topology of a two-stage CMOS operational amplifier. The design parameters are listed as follows:  $(W/L)_1 = (W/L)_2 = 20 \mu\text{m}/0.8 \mu\text{m}$ ,  $(W/L)_3 = (W/L)_4 = 5 \mu\text{m}/0.8 \mu\text{m}$ ,  $(W/L)_6 = 10 \mu\text{m}/0.8 \mu\text{m}$ ,  $(W/L)_5 = (W/L)_7 = (W/L)_8 = 40 \mu\text{m}/0.8 \mu\text{m}$ ,  $I_{REF} = 90 \mu\text{A}$ ,  $V_{in} = 0.7 \text{ V}$ ,  $V_{tp} = -0.8 \text{ V}$ ,  $\mu_n C_{ox} = 160 \mu\text{A/V}^2$ ,  $\mu_p C_{ox} = 40 \mu\text{A/V}^2$ ,  $|V_A| = 9 \text{ V}$  for all devices,  $V_{DD} = V_{SS} = 2.5 \text{ V}$ . The total capacitances between the output and ground is  $C_2 = 2 \text{ pF}$ .

- 2-1 Find the dc open-loop voltage gain. (6 分)
- 2-2 Find the value of  $C_C$  that results in unit-gain frequency  $f_t = 10 \text{ MHz}$ . And also find the corresponding frequencies of transmission zero  $f_z$  and second pole  $f_{p2}$ . (6 分)
- 2-3 If a resistor  $R$  is placed in series with  $C_C$ , find the value of  $R$  to obtain the transmission zero to be located at infinite frequency. (6 分)

3. 計算題與簡答題 (14 分)

Figure 3 shows a second order filter which is realized using the op-amp RC resonator.  $K$  is the voltage gain of buffer amplifier. The design parameters of this filter are listed as follows:  $R_1 = R_2 = R_3 = R_5 = 13.25 \text{ k}\Omega$ ;  $R_6 = 265 \text{ k}\Omega$ ;  $C_4 = C_6 = 1.2 \text{ nF}$ .

- 3-1 Please identify the filter type. (2 分)
- 3-2 What are the equivalent inductor value  $L$  and pole  $Q$  factor of the resonator? (6 分)
- 3-3 What are the pole frequency  $\omega_0$  and its 3-dB bandwidth of this filter? (6 分)

注意：背面有試題

4. 設計題 (10 分)

Fig. 4 shows a NMOS network of a static CMOS logic gate with five input signals A, B, C, D, E and output node F. Design and complete the full transistor circuit for this static CMOS logic gate to perform a complemented function. (10 分)

所別：電機工程學系碩士班 甲組(一般生) 科目：電子學  
甲組(學位在職生)

5. 設計題 (10分)

Design a complementary CMOS gate to perform the logic function  $C_1$  as shown in Fig. 5. (10分)

6. 設計題 (12分)

Figure 6 shows a multi-output domino logic circuit. Can you find out the output logic functions of  $C_3$ ,  $C_2$  and  $C_1$ ? (12分)

7. 計算題 (8分)

Determine the dynamic power dissipated for a typical CMOS clock driver with a 3 pF capacitance loading when operated at a frequency of 400 MHz and  $V_{DD}$  is 2.5 volts. (8分)

8. 說明題 (10分)

Draw a PN junction cross-section view includes the electrical field, potential voltage and positive/negative charges in the junction. (10分)

 


Fig. 3

 


Fig. 4

 


Fig. 5

 


Fig. 6