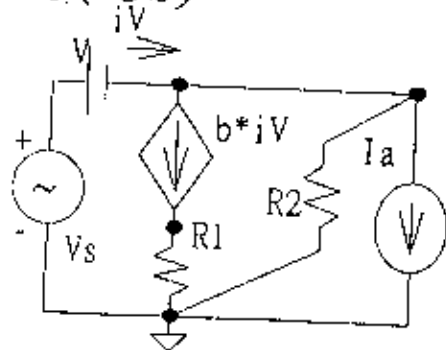


國立中央大學九十一學年度碩士班研究生入學試題卷

所別: 機械工程學系 成組 科目: 動力學及電路電子學 共 1 頁 第 1 頁

1. (25分)



- (1) 試利用這個電路來說明“加成定理成立”。
- (2) 假設 $b=7, R_1=2, R_2=3$, 試求電流源 I_a 所感受到的電路的等效電路, 亦即電路中除了 I_a 之外的元件對 I_a 而言的等效電路。

2. (25分)


Design the bandpass filters with the bandwidth $B \approx 500$ Hz, low half-power frequency $f_l = 100$ Hz, and high half-power frequency $f_H = 600$ Hz by

- (a) (20%) Connecting a first-order lowpass filter and highpass filter in cascade. Show the overall circuit and transfer function. Sketch the Bode magnitude and phase plot.
- (b) (20%) Using a RLC resonant circuit. Show the overall circuit and transfer function. Sketch the Bode magnitude plot.

3. (25分)


The bob of a simple pendulum of length $l=800$ mm is released from rest when $\theta=5^\circ$. Assuming simple harmonic motion, determine 1.6 s after release

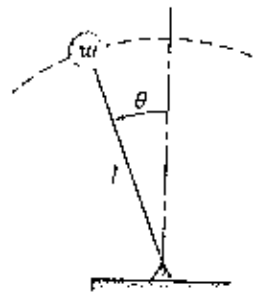- (a) the angle θ , (12%)
- (b) the magnitude of the velocity and acceleration of the bob. (13%)



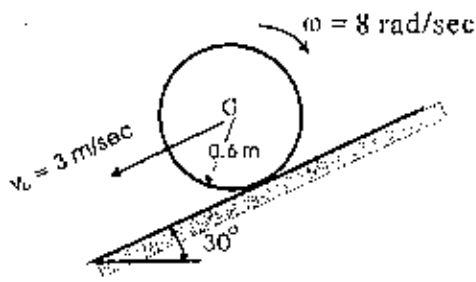4. (25分)

The thin ring has a mass of 5 kg and is released down the inclined plane such that it has a backspin $\omega=8$ rad/sec and its center has a velocity $v_C=3$ m/sec as shown. If the coefficient of friction between the ring and the plane is $\mu_k=0.6$, determine how long (in sec) the ring rolls before it stops slipping. (除了寫出解題過程外, 請務必以幾行文字具體說明處理此問題的原則或原理)



參考用