

# 國立中央大學108 學年度碩士班考試入學試題

所別： 光電類

共 2 頁 第 1 頁

科目： 電子學

本科考試可使用計算器，廠牌、功能不拘。

本試題共四大題計算題。 計算題需計算過程，無計算過程者不予計分

1. Design an active filter. According to Fig. 1, please answer the following questions.

- 2% (a) Please give the types of filter corresponding to the circuits shown in Fig. 1(a) and 1(b).
- 10% (b) If  $R_1 = R_2 = R_3 = R_4 = 100 \Omega$  and  $C_1 = C_2 = 1 \mu F$ , please give the transfer functions  $H_1(\omega)$  and  $H_2(\omega)$  for Fig. 1(a) and 1(b) and draw the corresponding magnitude Bode plots for each transfer function.
- 6% (c) Design task 1: Design an active band-pass filter with central frequency at 1000 rad/s and a maximum gain of 5 at the central frequency. Please give the circuit of this band-pass filter and the value of each element.
- 3% (d) According to the circuit designed in (c), please give its transfer function and explain why this circuit can match the goal in (c).
- 6% (e) Design task 2: Design an active non-inverting low-pass filter with corner frequency at 1000 rad/s and a gain of 5 within the passband. Please give the circuit of this band-pass filter and the value of each element.
- 3% (f) What are the differences between passive and active filter? Please list the differences as more as possible

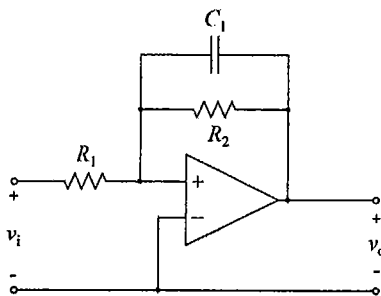


Fig. 1(a)

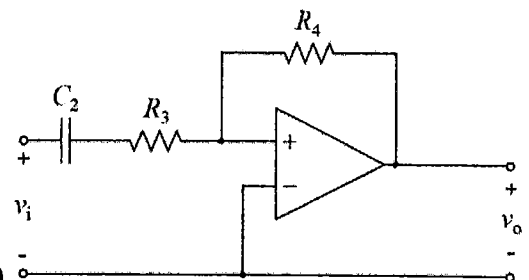


Fig. 1(b)

- 5% 2. Please give the reason why close-loop gain is preferred rather than open-loop gain for using Op Amp?
- 15% 3. Use Op Amp circuit to synthesize a signal  $s(t) = 4 \cos(1000t) - 5 \cos(500t) - 2 \cos(100t)$  with three given signal sources  $\cos(1000t)$ ,  $\cos(500t)$  and  $\cos(100t)$ . According to the circuit in Fig. 2, please give the values of  $R_1$ ,  $R_2$  and  $R_3$ , and three inputs of  $v_1(t)$ ,  $v_2(t)$  and  $v_3(t)$  to achieve the output of  $s$ .

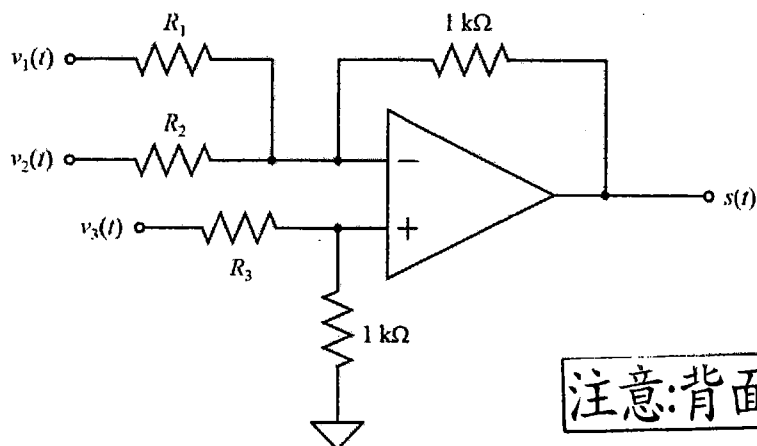


Fig. 2:

注意:背面有試題

所別： 光電類

科目： 電子學

本科考試可使用計算器，廠牌、功能不拘。

4. Consider the circuit shown in Fig. 3. The parameters are  $\beta = 180$ , and the Early voltage  $V_A = \infty$ ,  $v_{o1} = v_{o2} = 2V$  and  $v_{o4} = 6V$  when  $v_1 = v_2 = 0V$ .

5%

(a) Determine the values of  $V_1$  and  $V_2$ ;

5%

(b) Determine the value of  $I_R$ ;

5%

(c) Determine the values of  $I_1$  and  $I_2$ , and explain the reason in details;

5%

(d) Determine the value of  $R_{C1}$ ;

5%

(e) Determine the value of  $R_{C2}$ ;

5%

(f) Determine the voltage gain  $A_v \equiv \frac{v_{o4}}{v_2}$ ;

10%

(g) Determine the differential-mode voltage gain  $A_{d1} \equiv \frac{(v_{o1} - v_{o2})}{(v_1 - v_2)}$ ;

10%

(h) Determine the differential-mode voltage gain  $A_d \equiv \frac{v_{o4}}{(v_1 - v_2)}$ .

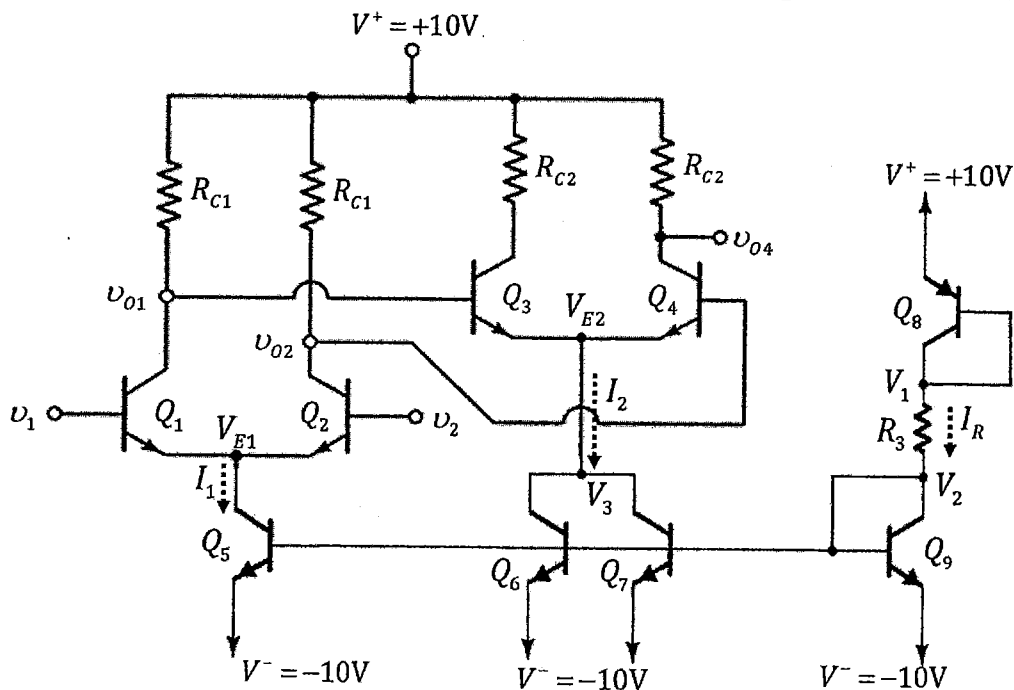


Fig. 3:

注意:背面有試題