

國立中央大學八十七學年度碩士班研究生入學試題卷

所別: 光電科學研究所 不分組 科目:

電子學

共二頁 第 1 頁

1(a) A logic inverter modeled as in Fig.1 employs a switch for which the offset voltage is 100 mV and the on resistance is 100 Ω . If the inverter load resistance is 1 K Ω and V^+ is 5 V, what are the two expected values of the output voltage? (10分)

(b) For a particular logic family for which the supply voltage is V^+ , $V_{OL} = 0.1V^+$, $V_{OH} = 0.8V^+$, $V_{IL} = 0.4V^+$, $V_{IH} = 0.6V^+$.

(1) What are the noise margins? (5分)

(2) What is the width of the transition region? (5分)

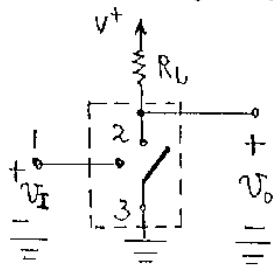


Fig. 1

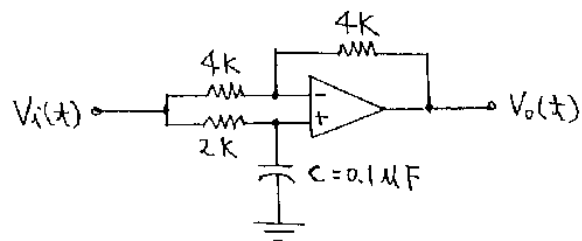


Fig. 2

2. For the operational amplifier shown in Fig.2. If the input voltage $V_i(t) = 5 \sin(2 \times 10^3 t)$, to find its corresponding output voltage $V_o(t)$? (20分)

3. Consider the emitter follower circuit of Fig.3. Find the values of R_1 and R_2 which will permit a maximum possible swing in the output. (20分)

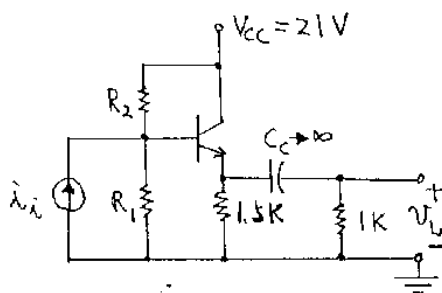


Fig. 3

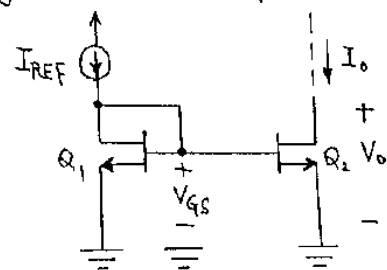


Fig. 4

參考

4. For the circuit shown in Fig. 4

(a) What kind of the MOSFET Q_1 and Q_2 (i.e. P-channel or n-channel? depletion-type or enhancement-type)? Draw the physical 3 dimensional structure Q_1 (5分)

(b) Draw the $i_D - V_{DS}$ characteristics of Q_1 (5分)

(c) Derive the relation between I_o and I_{REF} (10分) [Hint: $Q_1 \neq Q_2$]

注意: 背面有試題

國立中央大學八十七學年度碩士班研究生入學試題卷

所別：光電科學研究所

不分組 科目：

電子學

共二頁 第 2 頁

5 Figure 5 shows the MOSFET amplifier fed with an input signal source V_i , having a negligible resistance. Using high frequency π model.

(a) To find the transfer function $V_o(s)/V_i(s)$ (5分)

(b) In practical case, zeros or poles of the transfer function is dominate? Explain it! (5分)

(c) Sketch a Bode Plot for the gain magnitude. (5分)

(d) To find the gain-bandwidth product (5分)

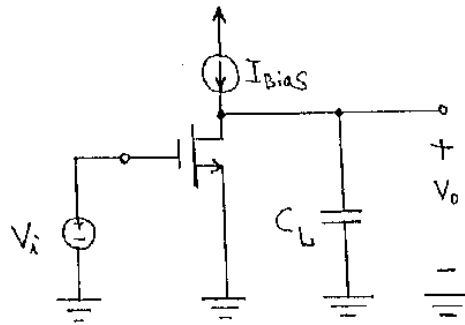


Fig. 5