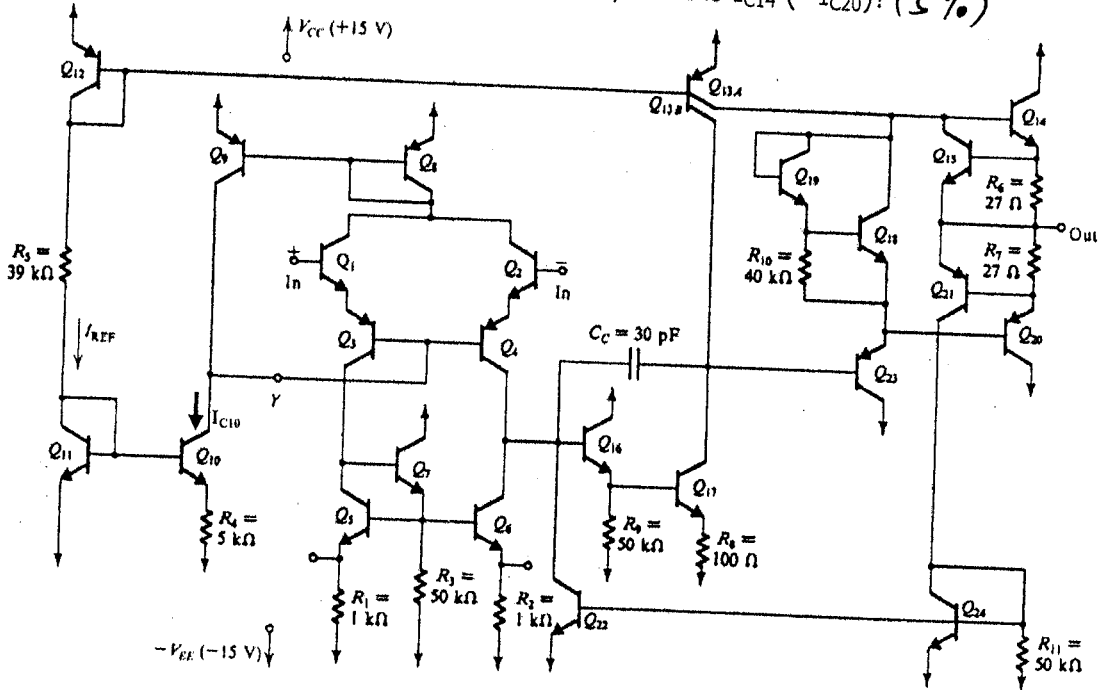


所別：光電科學研究所碩士班 一般生 科目：電子學


學位在職生

15 % 1. Refer to the circuit below, calculate the values of

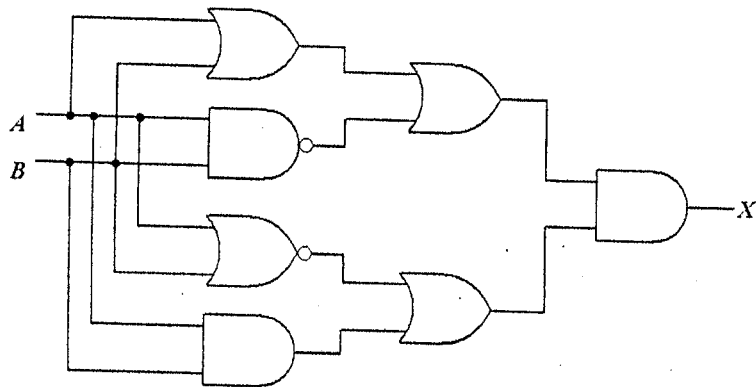- (a)  $I_{REF}$  (5%)
- (b)  $I_{C10}$  ( $I_C$  of  $Q_{10}$ ) (5%)
- (c) If  $I_{C13A} = 0.25 I_{REF}$  and  $V_{out} = 0.0$ , what is  $I_{C14}$  ( $=I_{C20}$ )? (5%)



15 % 2. Simplify the logic circuit with as few logic gates as possible (AND, OR, and NOT gates only).  $A$  and  $B$  are two input ports, and  $X$  is the output port.




15 % 3. Draw the circuit symbol and label the node's name : (a) Zener diode, (b) pnp BJT, (c) enhancement n-channel MOSFET, (d) depletion p-channel MOSFET, (e) p-channel JFET. (3x5=15)


注意：背面有試題

所別：光電科學研究所碩士班 一般生 科目：電子學  
學位在職生

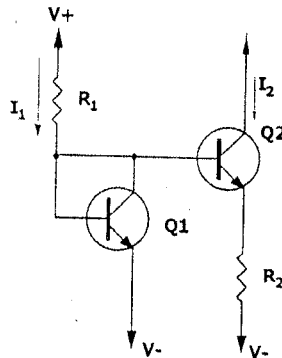15% 4. Derive the relation between  $I_1$  and  $I_2$  in the circuit below.



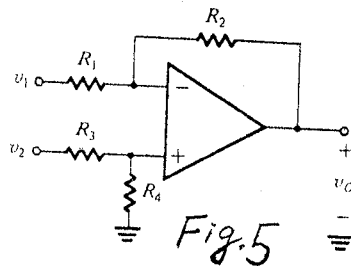20 % 5. Consider the difference amplifier of Fig. 5 with the two input terminals connected together to an input common-mode single source. For  $R_2/R_1 = R_4/R_3$ , show that the input common-mode resistance is  $(R_3 + R_4) \parallel (R_1 + R_2)$



20% 6. Show that if all transistors are operated at an effective voltage  $V_{eff}$  and have equal Early voltage  $|V_A|$ , the gain is given by

$$A_d = 2(V_A / V_{eff})^2 \quad (10\%)$$

Evaluate the gain for  $V_{eff} = 0.25$  V and  $V_A = 20$  V. (10%)

