

類組：電機類 科目：數位邏輯(300H)

共 9 頁 第 1 頁

※請在答案卷內作答

考生請注意：

- 本試卷共有 20 題試題。每題 5 分。
- 你的答案必須如下圖所示由上而下依序寫在答案卷的作答區。
- 只要填寫考題所要求的答案，請勿附加計算過程。

從此處開始寫起

1. (a), (b).

2. (c), (d).

3. 15

4. (1) 1, (2) 0

5. $Z = B + AC'$

、 、 、

注意：背面有試題

※請在答案卷內作答






Question 1 [5pt]. Determine the radix r for the following equation:

$$(13)_r \times (21)_r - (24)_r = (244)_r.$$

Question 2 [5pt]. Let $(N)_R$ denote the number N under radix R , and omit specifying the radix when $R = 10$. What should be the number in radix 10 corresponding to $(11)_{(11)(11)(11)(11)_2}$?

Question 3 [5pt]. If we already know that $A \oplus B \oplus C \oplus D = 1$, then $ABC + ABD + ACD + BCD = 1$. True or False?

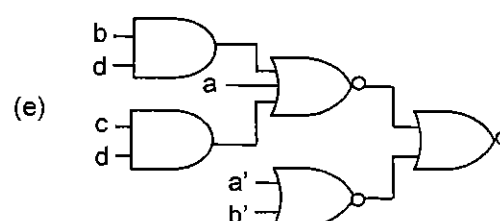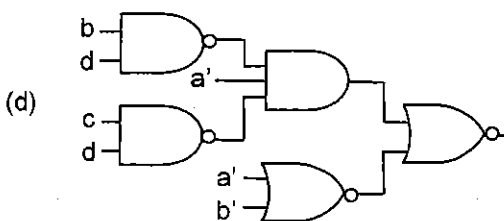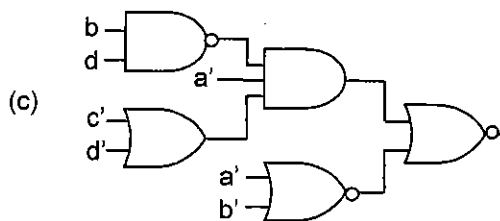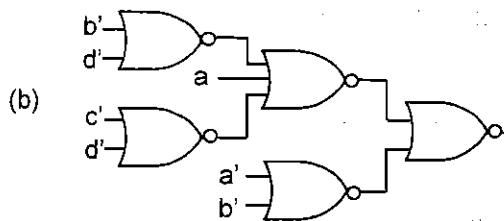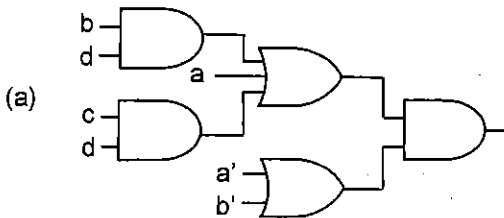Question 4 [5pt]. Consider circuit (a), which of the four circuits (b)~(e) are equivalent to (a)?



Question 5 [5pt]. Consider a logic operation: $X \otimes Y = XY + X'$. Is the operation “ \otimes ” functionally complete?

Question 6 [5pt]. Given the maxterm expansion of a 3-input function $F = M_0 \bullet M_3 \bullet M_6$. Represent F' (complement of F) and F^D (duality of F) by minterm expansion.

Question 7 [5pt]. The maxterm expansion of the complement of F is given by

$$F'(a, b, c, d) = \Pi M(1, 3, 4, 8, 10, 11, 12, 15) \bullet \Pi D(0, 14).$$

Please write down the **minimum** sum of products for function F .


注意：背面有試題

參考用

※請在答案卷內作答

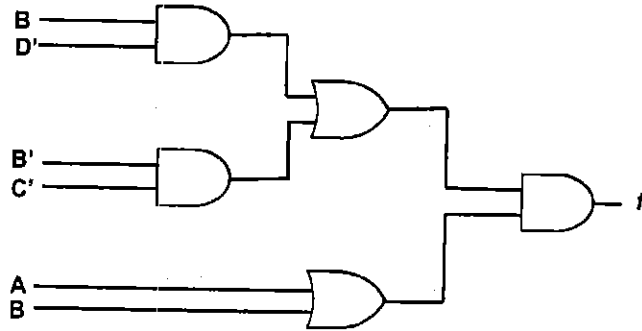
Question 8 [5pt].

Consider the following three-level circuit. How many possible static hazards are in this circuit?



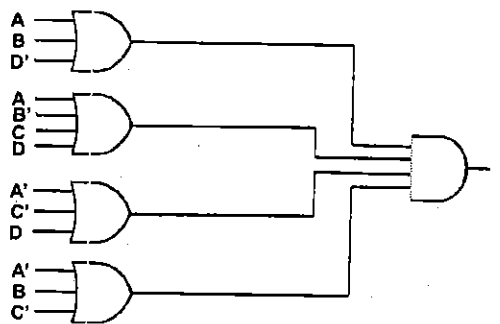
Question 9 [5pt].

Please identify the input transition that could cause static 0-hazard to the following circuit.



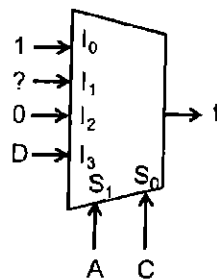Question 10 [5pt].

The following 4-to-1 MUX implements the function: $f(A,B,C,D) = A'C' + A'B'D' + ACD + A'BD$. Please identify the missing input signal I_1 .



參考用


Question 11 [5pt].

Please derive the Boolean algebra equation for the next value of the output Q in terms of Q, A, and B.

$Q^+ = \underline{\quad} + \underline{\quad}$

注意：背面有試題


※請在答案卷內作答

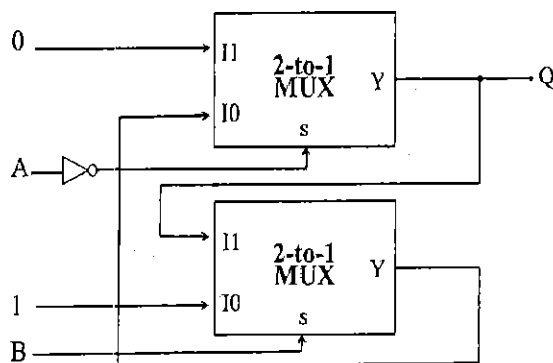

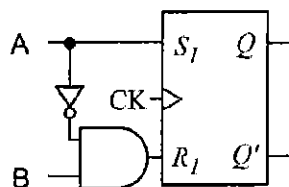Question 12 [5pt].

The following circuit uses a S-R Flip-Flop to implement a special type of Flip-Flop. Please derive the next-state equation of the output Q.

$Q^+ = \underline{\hspace{2cm}} + \underline{\hspace{2cm}}$



Question 13 [5pt].

A U-V flip-flop operates as follows. If $UV = 00$, the flip-flop does not change state. If $UV = 10$, the flip-flop is set to $Q = 0$. If $UV = 11$, the flip-flop changes state. The input combination $UV = 01$ is not allowed. Please derive the next-state equation of this flip-flop.

$Q^+ = \underline{\hspace{2cm}} + \underline{\hspace{2cm}}$

Question 14 [5pt].

A decade counter counts in the sequence: 0000, 0001, 0010, 0011, 0100, 0101, 0110, 0111, 1000, 1001, (repeat) 0000,

Design this counter using J-K flip-flop. What is the next state if the counter is started in state 1101?

Question 15 [5pt]. Figure-1 illustrates a Mealy machine with two JK flip-flops (A and B) and some logic circuits with the logic expressions denoted as L-a, L-b and L-c. Figure-2 shows the state transition graph of this mealy machine, where S_0, S_1, S_2 and S_3 represent $(A,B) = (0,0), (0,1), (1,0)$ and $(1,1)$, respectively.

注意：背面有試題

參考用

※請在答案卷內作答

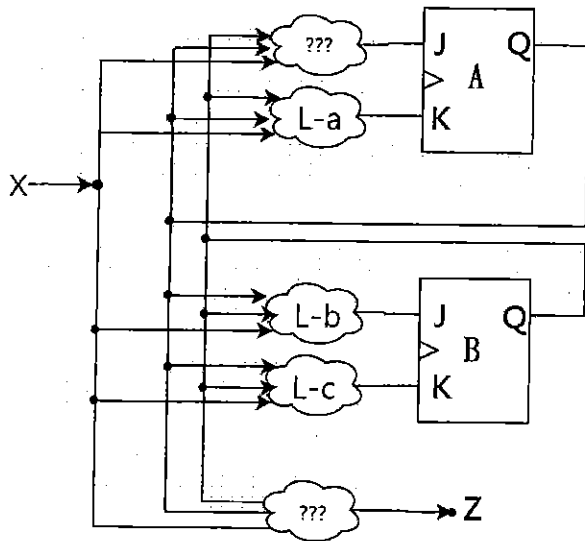


Figure-1

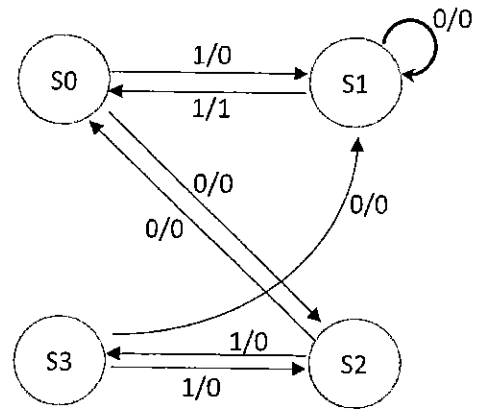


Figure-2

Which of the following ten logic expressions can meet the specification of the mealy machine defined above?

- (1) $L-a = B'X$ (2) $L-a = BX'+B'X$ (3) $L-a = BX+B'X'$ (4) $L-a = A BX'+AB'X$
 (5) $L-b = X$ (6) $L-b = AX$ (7) $L-b = A'X$ (8) $L-c = X$
 (9) $L-c = X'$ (10) $L-c = A'X$

Question 16 [5pt]. Table-1 shows the state table of a Moore machine with one input (X), two outputs (Z_0 and Z_1) and three flop-flops. Output (Z_0, Z_1) represents the binary number of the sum of the last three inputs, where $(Z_0, Z_1) = (0, 0), (0, 1), (1, 0), (1, 1)$ denotes 0, 1, 2, and 3. Eight states, denoted by S_0, S_1, S_2, \dots and S_7 , represents 000, 001, 010 ... and 111 of the last three inputs, respectively. There are five missing slots (from a to e) in the state table. Table-2 shows an exemplary input sequence and its corresponding output sequence.

state	Next state		$Z_0 Z_1$
	$X=0$	$X=1$	
S_0	S_0	S_1	00
S_1	a	S_3	01
S_2	S_4	b	01
S_3	S_6	S_7	d
S_4	S_0	c	01
S_5	S_2	S_3	e
S_6	S_4	S_5	10
S_7	S_6	S_7	11

Table-1



注意：背面有試題

※請在答案卷內作答

X	0	1	1	0	1	1	1	0	0	0
Z0 Z1	00	01	10	10	10	10	11	10	01	00

Table-2

Which of the following statements about the missing slots are true for the given Moore machine?

- (1) a=S1 (2) a=S2 (3) b=S0 (4) c=S1 (5) c=S5
 (6) d=01 (7) d=10 (8) e=01 (9) e=10

Question 17 [5pt]. Table-3 shows the state assignment for two flip-flops (denoted as A and B) of a mealy machine with one input X and one output Z, where $Z=1$ whenever input sequence 010 occurs at X. Table-4 shows an exemplary input sequence and its corresponding output sequence.

AB	Continuous sequence in
00	none
01	0
10	01

Table-3

X	0	0	1	0	1	0	1	1
Z	0	0	0	1	0	1	0	0

Table-4

Which of the following five circuits can realize the Mealy machine defined above?

注意：背面有試題


參考用

類組：電機類 科目：數位邏輯(300H)


共 9 頁 第 7 頁

※請在答案卷內作答


(a)

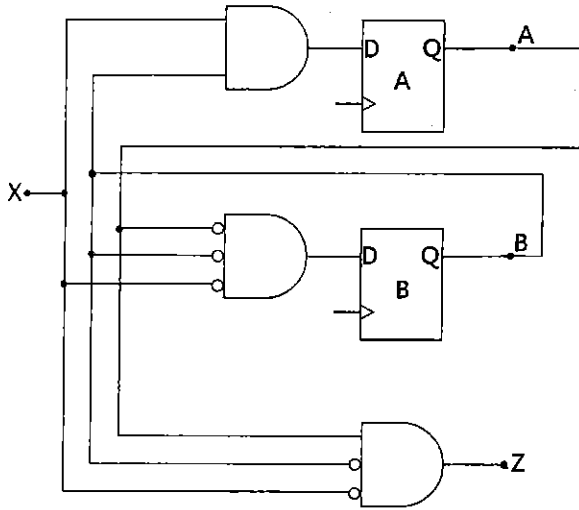


(b)

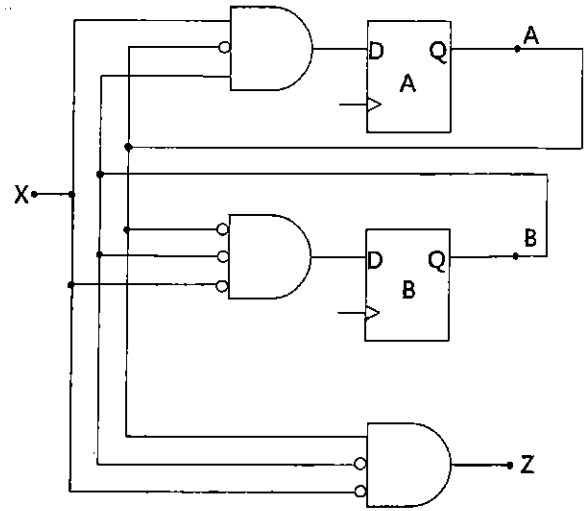


(c)

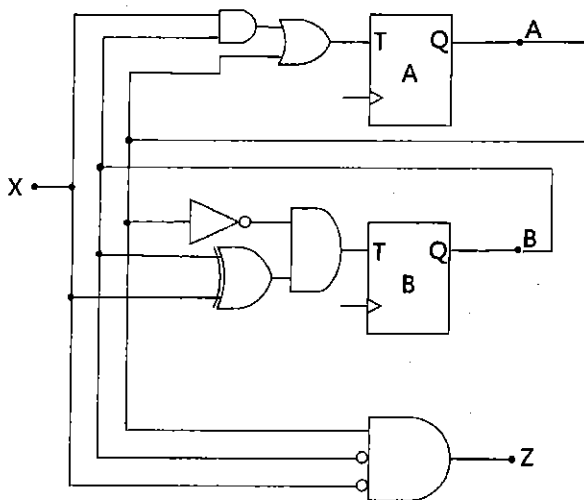

(d)

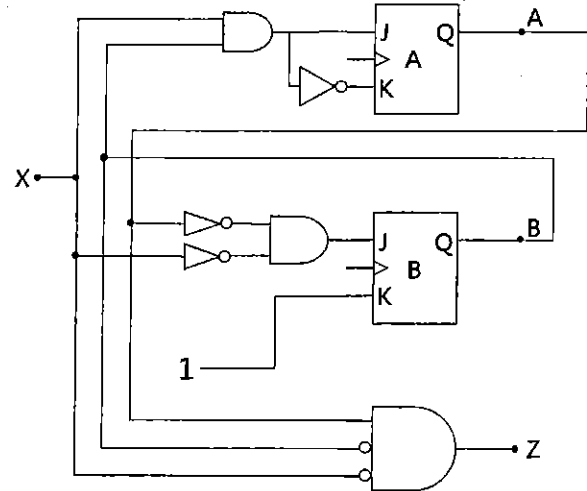

(e)

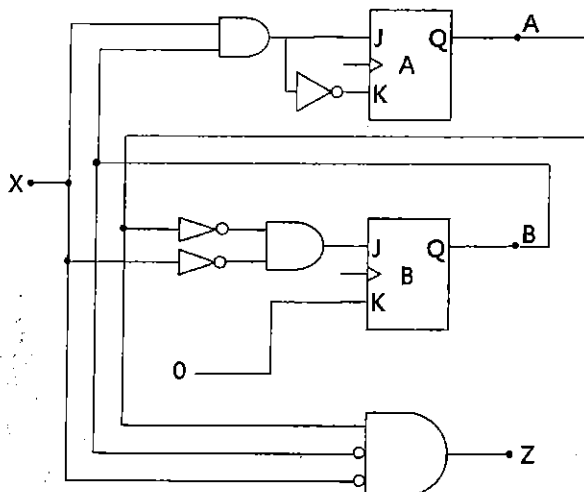

注意：背面有試題

參考用

※請在答案卷內作答

Question 18 [5pt]. Reduce the following state table (Table-5) to the minimum number of states. Please list all the equivalent states in the original state table. (For example, $i=j=k, l=m$.)

Present State	Next State		Present Output	
	X=0	X=1	X=0	X=1
a	h	c	1	0
b	c	d	0	1
c	h	b	0	0
d	f	h	0	0
e	c	f	0	1
f	f	g	0	0
g	g	c	1	0
h	a	c	1	0

Table-5

Question 19 [5pt]. Figure-3 shows the state graph representing a sequential circuit that controls a binary multiplier. The circuit contains three inputs (St, M, and K) and four outputs (Load, Ad, Sh, and Done). A one-hot state assignment with four flip-flops (denoted as Q_0, Q_1, Q_2 and Q_3) is used to represent each of the four states. The one-hot assignment for each state is also listed in Figure-3.

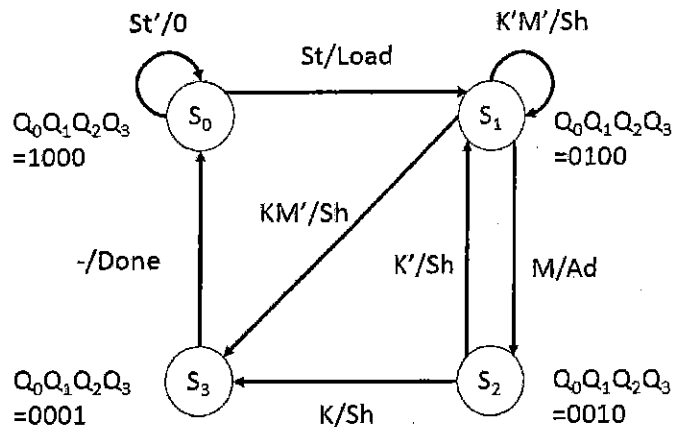


Figure-3

參考用

Represent the next state of Q_1 (denoted as Q_1^+) and the output Sh with a logic expression of the present states of the four flop-flops and the inputs. The reported logic expression must be reduced to the minimum sum of product.

注意：背面有試題

※請在答案卷內作答

Question 20 [5pt]. Figure-4 shows a counter using three T flip-flops, A, B, and C. The counter will generate the following repeated sequence: $ABC = 000 \rightarrow 111 \rightarrow 110 \rightarrow 001 \rightarrow 011 \rightarrow 000 \rightarrow 111 \dots$ (repeat).

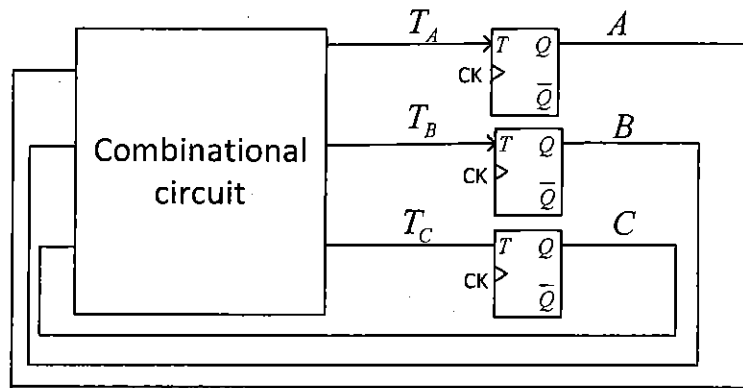


Figure-4

What is the **minimum sum of product** for each input equation of the three T flip-flops, T_A , T_B , and T_C ?

參考用